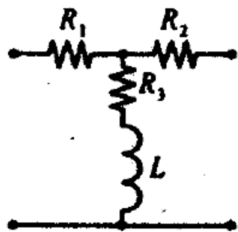


homework 4

For the following T-network inserted into a transmission line with characteristic impedance of $Z_0 = 50\Omega$, the three resistances are $R_1=R_2=8.56\Omega$, and $R_3=141.8\Omega$. Find the S-parameters of this configuration and plot the insertion loss as a function of inductance L for the frequency of $f=2\text{GHz}$ and L changing from 0 to 100nH.



当电路插入到无限长的传输线中后，其电路 1所示：

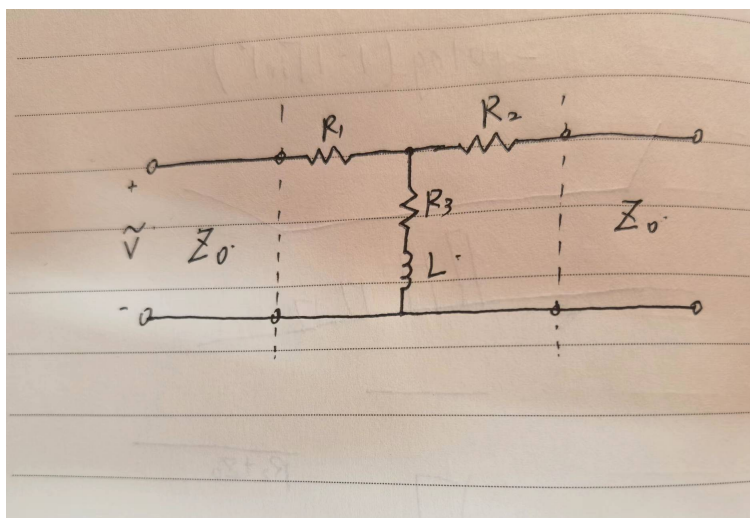


Figure 1: 电路图

通过从电压源正极看入，可以得到输入电阻：

$$Z_{in} = Z_0 + R_1 + \frac{1}{\frac{1}{R_2 + Z_0} + \frac{1}{R_3 + j\omega L}}$$

由此可得反射系数 $|\Gamma_{in}|$ ，也即 S11 参数：

$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

matlab 计算得到的结果如图 2所示：

ans =

$$(69095816858483726725 * L - 820747436032i) / (172039524931314070475 * L - 2462096556032i)$$

Figure 2: S11 计算值

对于 S21, 可以将其视为插入损耗, 其值可以通过 S11 计算得到:

$$S_{21} = -10\lg(1 - |S_{11}|^2)$$

根据以上计算, 借助 matlab 代码, 可以得到 S11 和 S21 随 L 的变化曲线:

```
1  %已知参数
2  syms L;
3  x=0:100;
4  l=x*10^(-9);
5  z0=50;
6  r1=8.56;
7  r2=8.56;
8  r3=141.8;
9  f=2e9;
10
11 %输入阻抗
12 zin=z0+r1+1./(1./(1i.*2.*pi.*f.*l+r3)+1./(r2+z0));
13 zin1=z0+r1+1./(1./(1i.*2.*pi.*f.*L+r3)+1./(r2+z0));
14
15 %S11参数
16 S11_1=(zin1-z0)./(zin1+z0);
17 simplify(abs(S11_1))
18 gin=(zin-z0)./(zin+z0);
19 S11=20*log10(abs(gin));
20 figure(1);
21 plot(x,S11);
22 title("S11参数变化曲线");
23 xlabel("L/nH");
24 ylabel("S11(dB)");
25
26 %S21参数
27 S21=-10.*log10(1-abs(gin).^2);
28 figure(2);
29 plot(x,S21);
30 title("S21参数变化曲线");
31 xlabel("L/nH");
32 ylabel("S21(dB)");
```

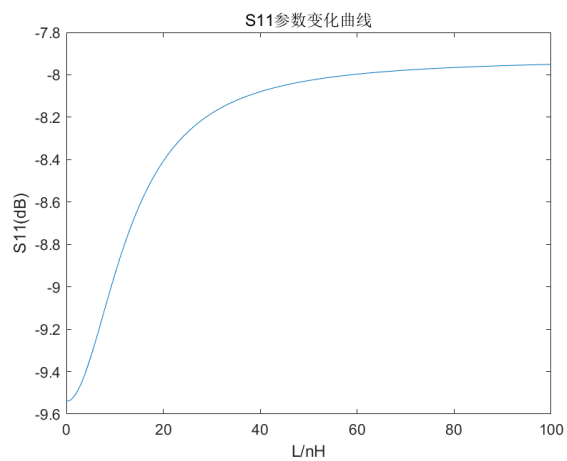


Figure 3: S11 变化曲线

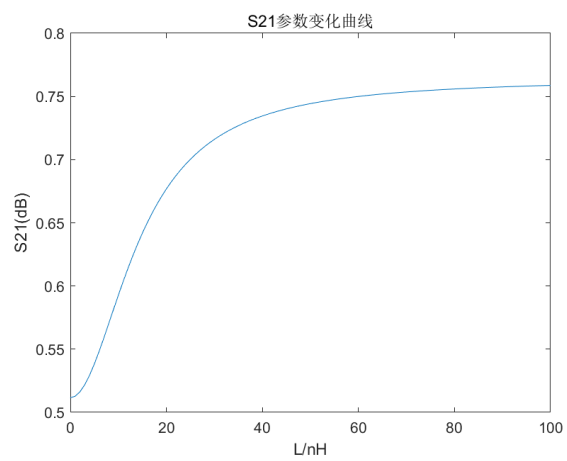


Figure 4: S21 变化曲线

从电路图中可以看出, 该电路有极高的对称性, 所以满足:

$$S_{11} = S_{22}, S_{21} = S_{12}$$

因此, S22 和 S12 不用重复计算。