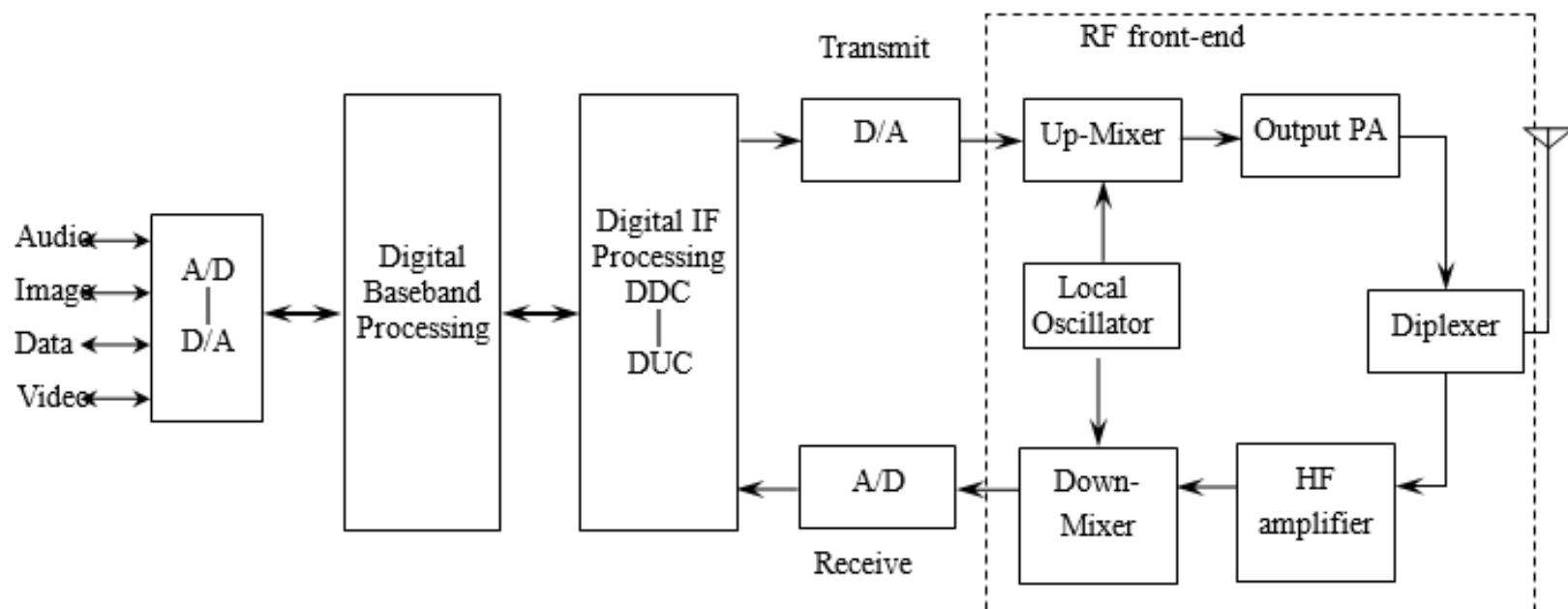



RF/Microwave Circuit and System

Lecture 2

System structure




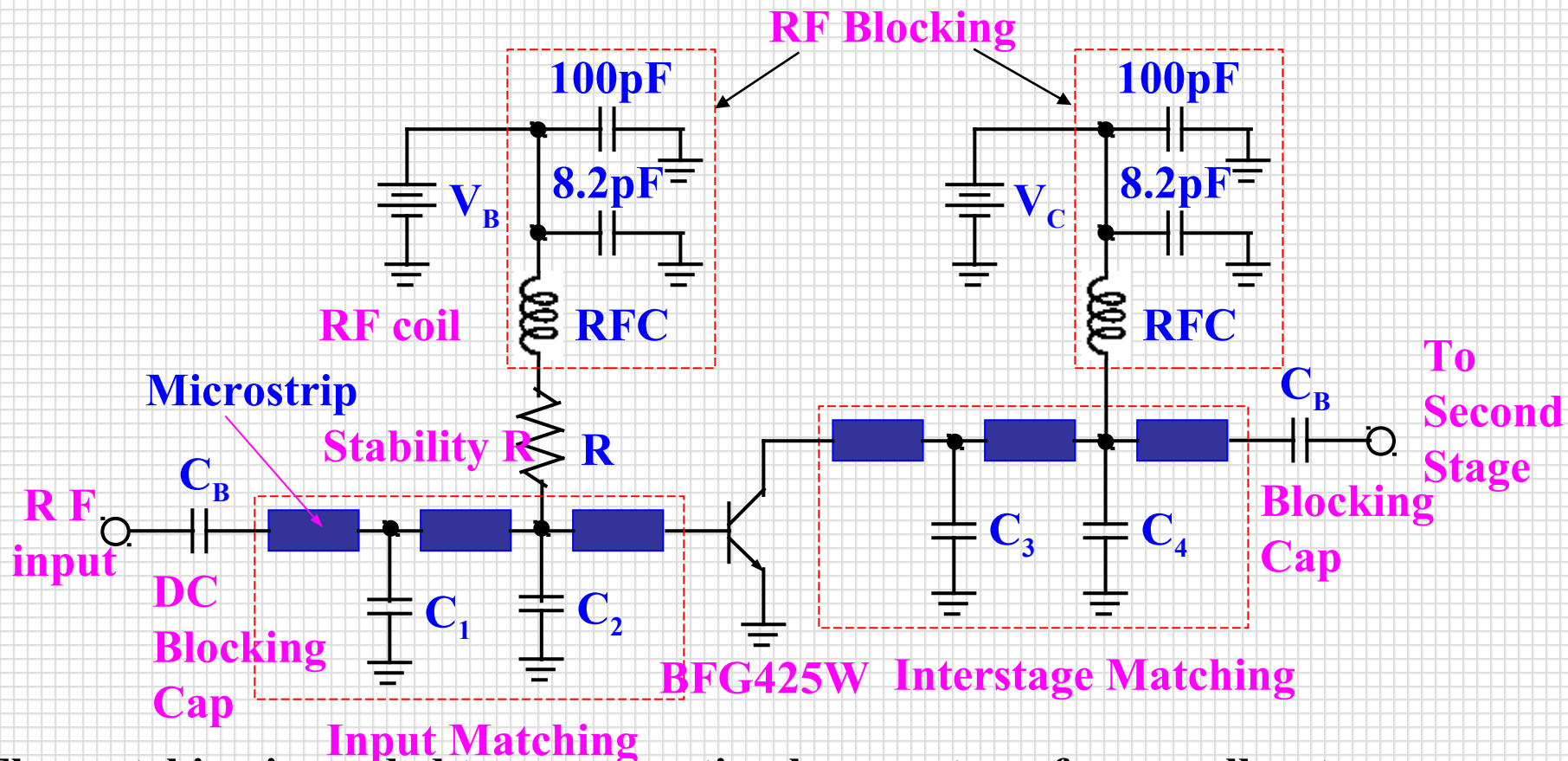2GHz first stage power amplifier for Mobile phone



The matching is needed to ensure optimal power transfer as well as to eliminate performance degrading reflections; The separation of high-Frequency signals from the DC bias conditions is achieved through two RF blocking networks (RFC)

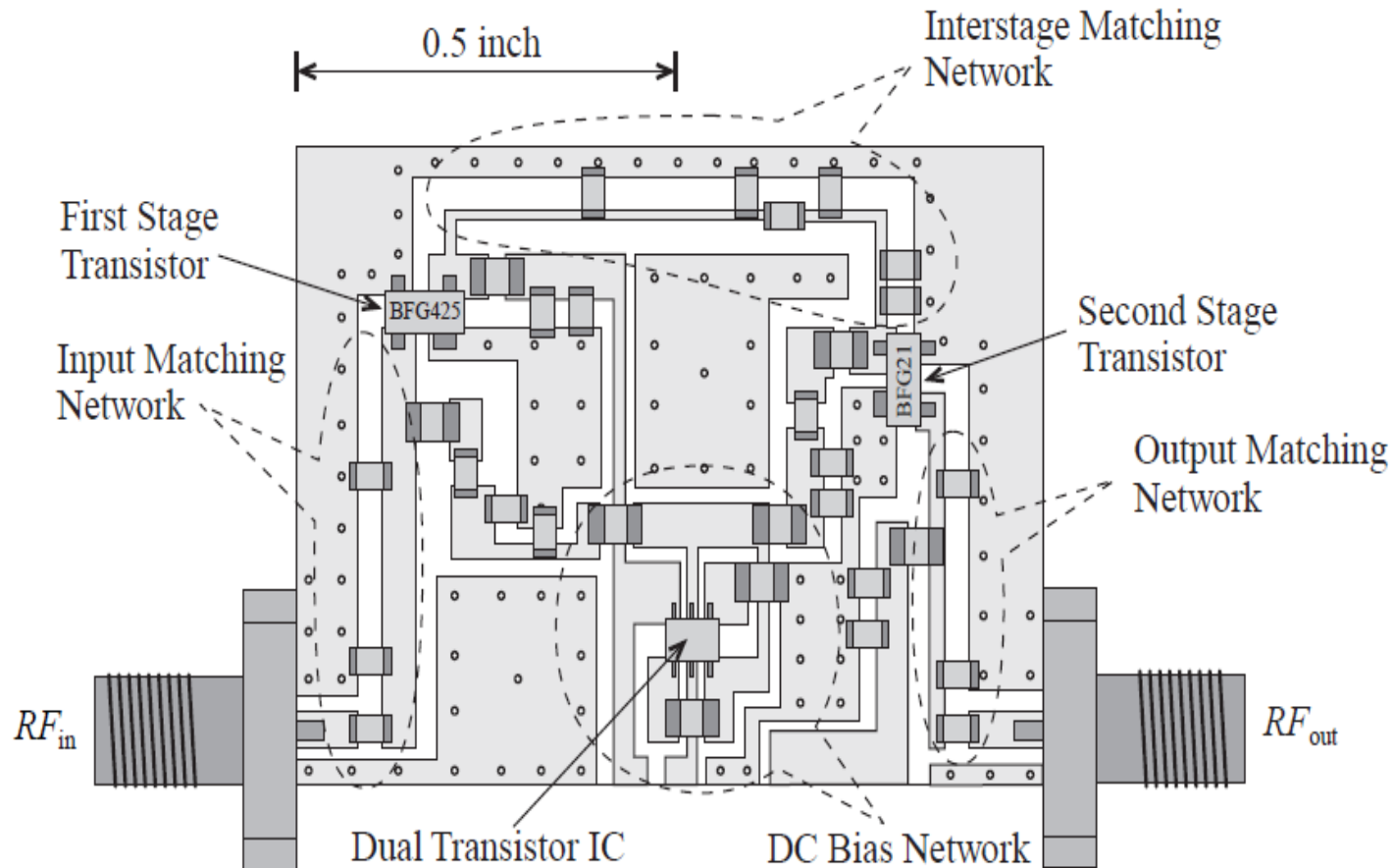Printed circuit board layout of the power amplifier.




To understand, analyze and ultimately build such a PA requires Knowledge of a number of RF topics

1.2 Dimensions and units

In free space, plane electromagnetic wave propagation in the positive **z**-direction

$$E_x = E_{0x} \cos(\omega t - \beta z) \text{ V/m} \quad \text{x-directed electric field vector}$$
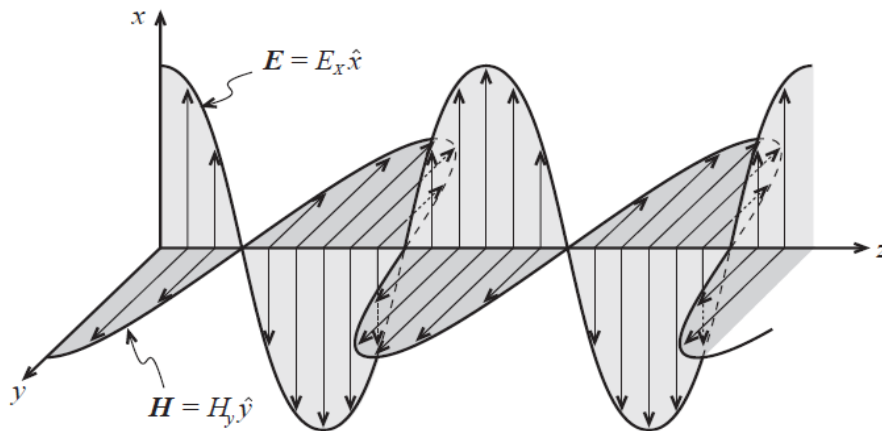
$$H_y = H_{0y} \cos(\omega t - \beta z) \text{ A/m} \quad \text{y-directed magnetic field vector}$$



Feature of plane wave :

Transverse electromagnetic mode ,

E and **H** are orthogonal to the direction of propagation

E and **H** are orthogonal to each other and same phase

Based on Maxwell , intrinsic impedance Z_0

$$Z_0 = E_x / H_y = \sqrt{\mu / \varepsilon} = \sqrt{(\mu_0 \mu_r) / (\varepsilon_0 \varepsilon_r)} = 377 \Omega \sqrt{\mu_r / \varepsilon_r}$$

Permeability μ and permittivity ε based on material ,

$\mu_0 = 4\pi \times 10^{-7} (\text{H/m})$, $\varepsilon_0 = 8.85 \times 10^{-12} (\text{F/m})$, μ_r and ε_r are relative values.

In the direction of wave propagation, the change of the phase Kz of the unit distance is called the phase constant (propagation constant).

$$\beta = k = \omega \sqrt{\mu \varepsilon}$$

Wavelength is the distance when kz changes 2π phase $\lambda = 2\pi / \beta$

Phase velocity is the speed of phase plane of sine wave .

$$\because \omega t - \beta z = \text{constant}, \text{ so } \omega dt - \beta dz = 0$$

\therefore phase velocity of TEM :

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta} = \lambda f = \frac{1}{\sqrt{\varepsilon \mu}} = \frac{c}{\sqrt{\varepsilon_r \mu_r}} \text{ m/s} \quad (1.3)$$

Transverse electromagnetic mode

Example 1.1 compute the intrinsic impedance ,phase velocity, and Wavelengths of an electromagnetic wave in free space for $f = 30\text{MHz}$, 300MHz , 30GHz

Solution : Relative permeability and permittivity of free space are equal to unity

Intrinsic impedance : $Z_0 = \sqrt{\frac{\mu}{\epsilon}} = \sqrt{\frac{\mu_0}{\epsilon_0}} = \sqrt{\frac{4\pi \times 10^{-7}}{8.85 \times 10^{-12}}} = 377\Omega$

Phase velocity : $v_p = \frac{1}{\sqrt{\epsilon\mu}} = \frac{1}{\sqrt{\epsilon_0\mu_0}} = 3 \times 10^8 \text{ m/s}$

wavelength : $\lambda = \frac{2\pi}{\beta} = \frac{2\pi v_p}{\omega} = \frac{v_p}{f} = \begin{cases} 10 \text{ m} \\ 1 \text{ m} \\ 1 \text{ cm} \end{cases}$

1.4 RF Behavior of Passive Components

Conventional circuit , R is f independent , $X_C = \frac{1}{\omega C}$, $X_L = \omega L$.

resistances, inductances, capacitances are not only created by wires, coils and plates, even a single straight wire or a copper segment of a PCB possesses frequency dependent R and L . DC resistance of a conductor :

$$R_{DC} = l / (\pi a^2 \sigma_{cond})$$

DC signal, the entire conductor cross-sectional area is utilized. At AC, the alternating charge carrier flow establishes a magnetic field that induces an electric field whose associated current density opposes the initial current flow. The effect is strongest at the center, the result is a current flow that tends to reside at the outer perimeter with increasing frequency — **Skin effect**

$$J_z = [p I J_0(pr)] / [2\pi a J_1(pa)]$$

$$p^2 = -j\omega\mu\sigma_{cond}, J_0, J_1$$

Z-directed current density :

where

are Bessel functions of zeroth and first order, and I

is the total current flow

in high freq ($f \geq 500\text{MHz}$) ,

Normalized R : $R/R_{\text{DC}} \cong a/2\delta$




Normalized L : $\omega L/R_{\text{DC}} \cong a/2\delta$

Skin depth : $\delta = (\pi f \mu_{\text{cond}})^{-1/2}$

Most case, for conductor $\mu_r = 1$,

Skin depth rapidly decreases for

Increasing frequencies

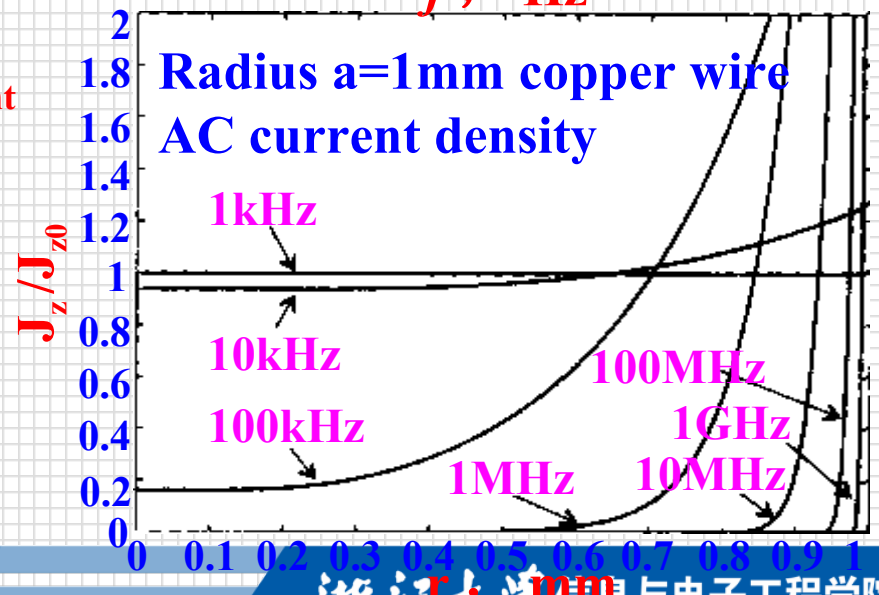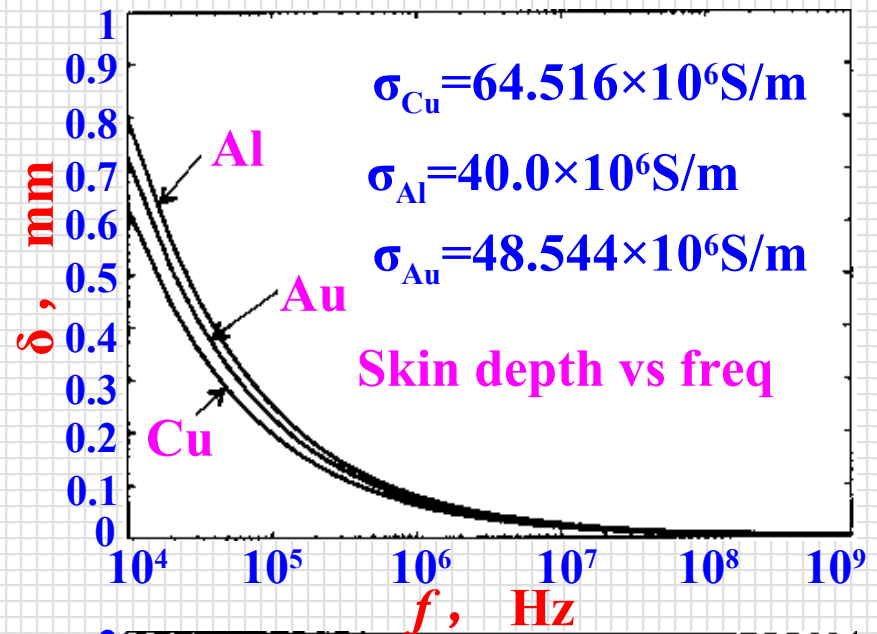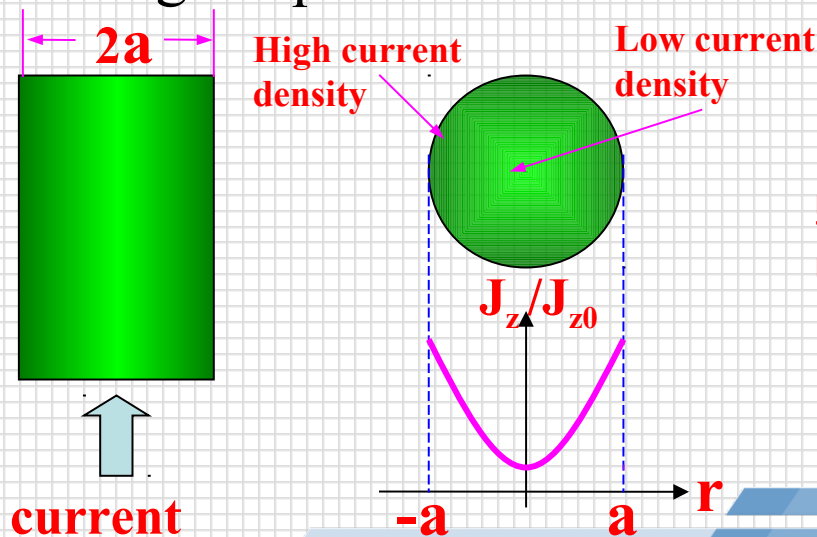

American wire gauge , diameter doubles every six wire gauges


AWG50 : $d=1\text{mil}$, AWG44 : $d=2\text{mil}$, AWG38 : $d=4\text{mil}$, ..

where : $1\text{mil}=2.54\times 10^{-5}\text{m}=2.54\times 10^{-2}\text{mm}$





1.4.1 High-frequency Resistors

In RF and MW circuits, thin-film chip resistors ,

Equivalent circuit :

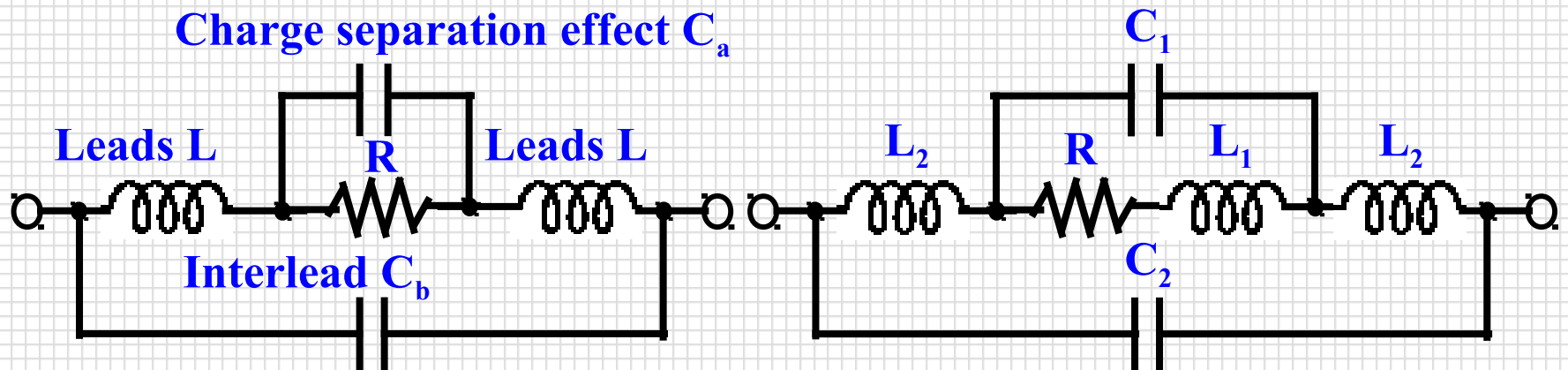

Equivalent circuit of the resistor Equivalent circuit of the wire-wound resistor

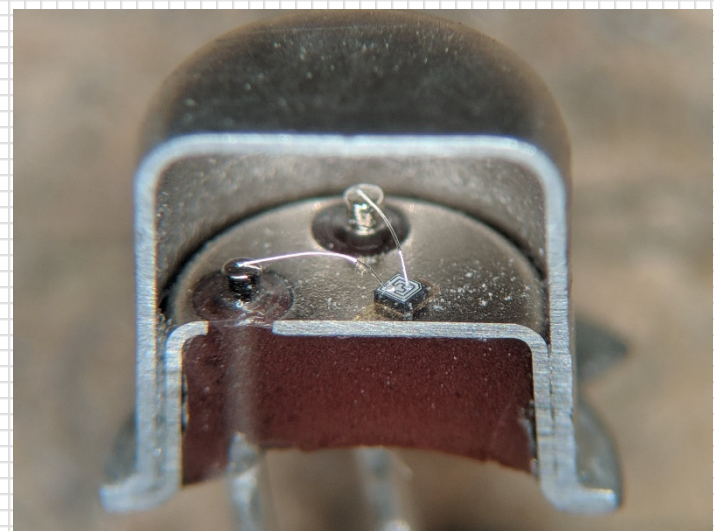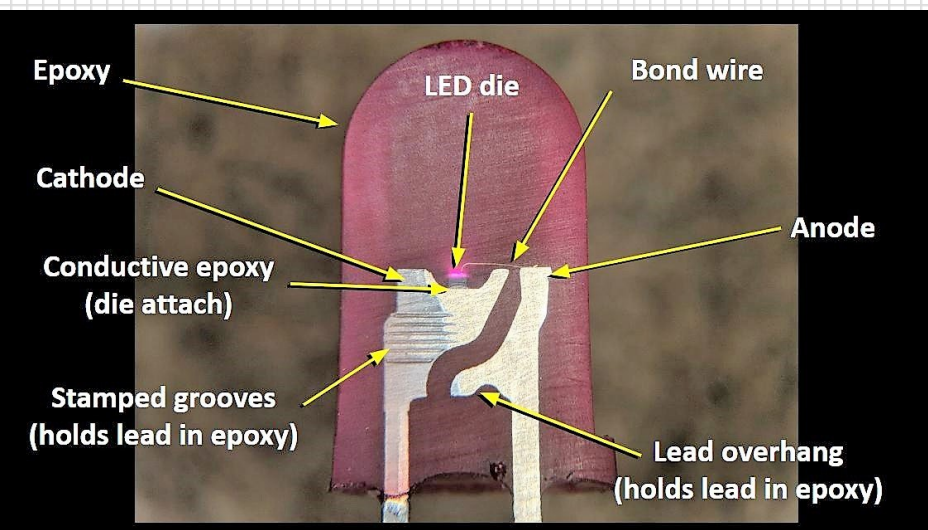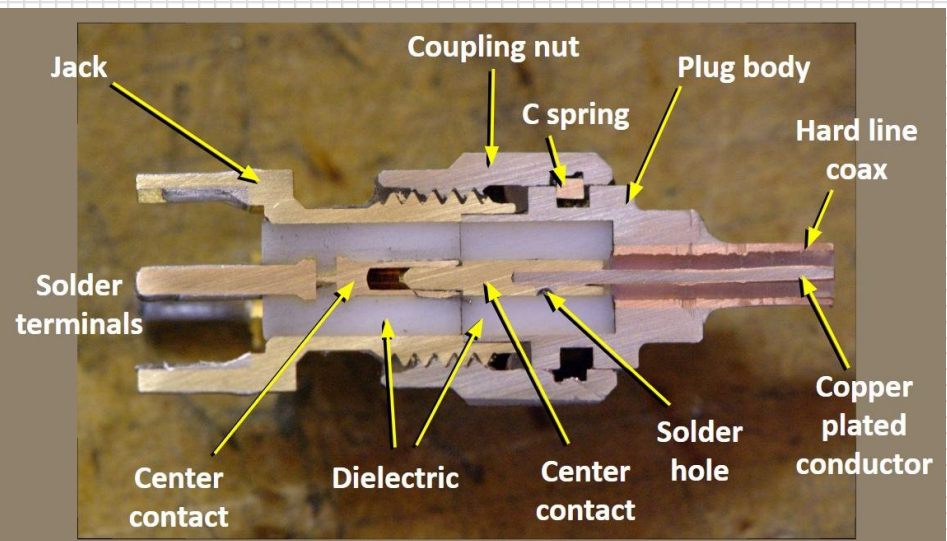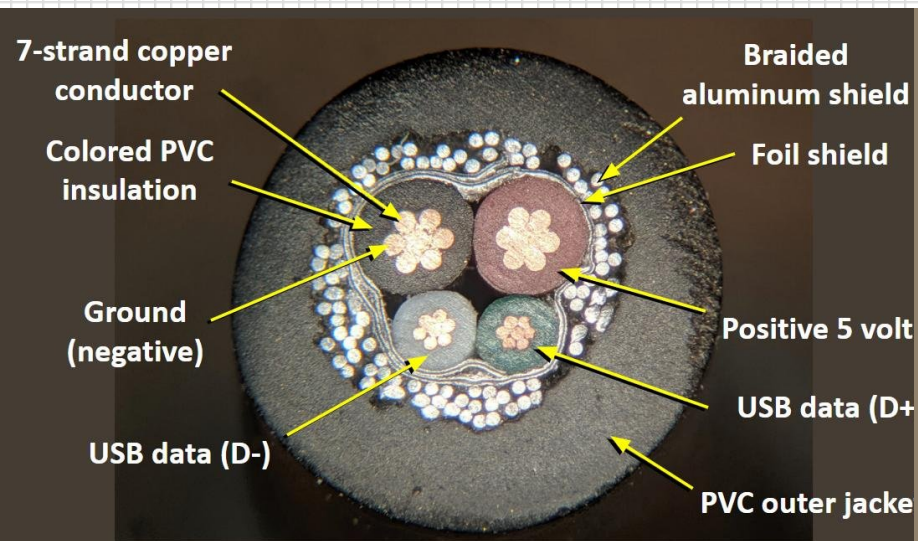

Example 1.3 find the high frequency impedance behavior of a 500Ω Metal film resistor with 2.5cm copper wire connections of AWG 26 And a stray capacitance $C_a=5\text{pF}$.

Solution : AWG26 $d=16\text{mil}$, $a=8\times 2.54\times 10^{-5}\text{m}=0.2032\text{mm}$ from 1.10 and 1.11 ,


$$L = \frac{aR_{DC}}{2\omega\delta_{Cu}} = \frac{a}{4\pi f} \frac{2l}{\pi a^2 \sigma_{Cu}} \sqrt{\pi f \mu_0 \sigma_{Cu}}$$

$$= \frac{0.25\sqrt{\mu_0}}{2a\pi\sqrt{\pi f \sigma_{Cu}}}$$

$$= \frac{0.125\sqrt{4\pi \times 10^{-7}}}{2.032 \times 10^{-4} \pi \sqrt{64.516 \times 10^6 \pi f}}$$

$$= \frac{1.54}{\sqrt{f}} \mu\text{H}$$
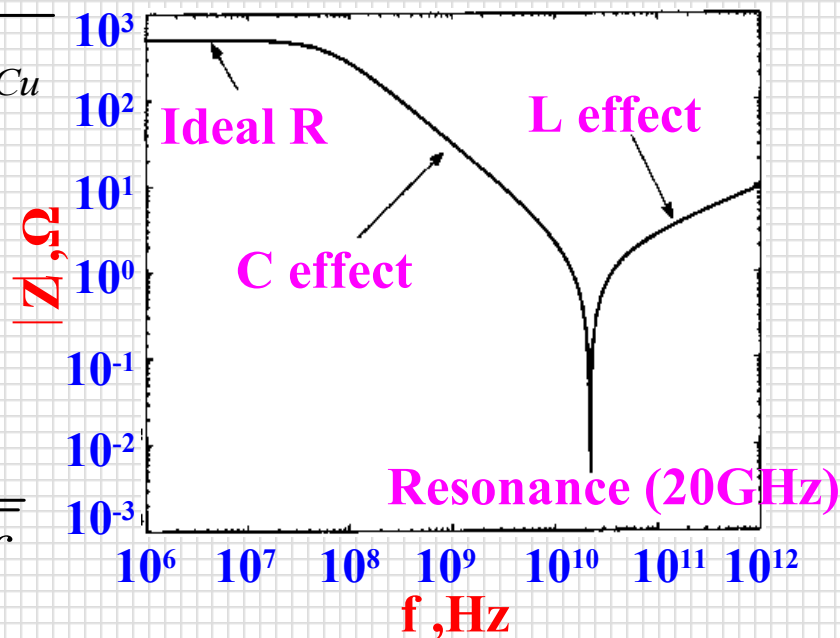
$$Z = j\omega L + \frac{1}{j\omega C + 1/R}$$



1.4.2 High-frequency Capacitors

In circuit analysis defines capacitance for a parallel plate with plate surface by the plate separation : $C = \frac{\epsilon A}{d}$


Ideally no current, at high freq, the dielectric material become lossy

Impedance of C : $Z = \frac{1}{G_e + j\omega C}$

where : $G_e = \frac{\sigma_{diel} A}{d}$, σ_{diel} dielectric, Series connection

series loss tangent $\tan \Delta_s = \frac{\omega \epsilon}{\sigma_{diel}}$

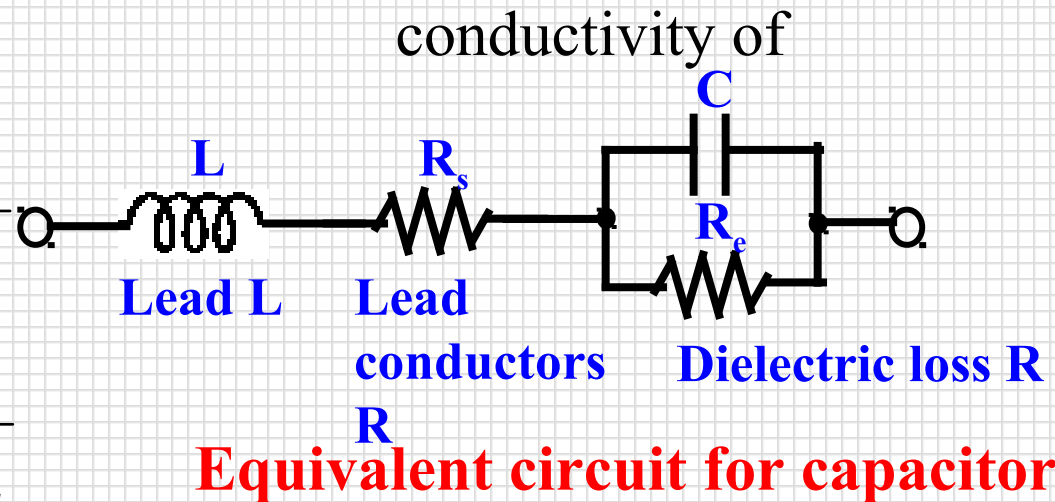Then : $G_e = \frac{\omega \epsilon A}{d \tan \Delta_s} = \frac{\omega C}{\tan \Delta_s}$



Equivalent circuit for capacitor

Examples 1.4 Compute the high frequency impedance of a 47pF Capacitor whose dielectric medium consists of an aluminum oxide possessing a series loss tangent of 10^{-4} and whose leads are 1.25cm AWG26 copper wires

Solution : similar example 1.3 , lead inductance :

$$L = \frac{aR_{DC}}{2\delta\omega} = \frac{2l}{4\pi a} \sqrt{\frac{\mu_0}{\pi\sigma_{Cu}f}} = \frac{771}{\sqrt{f}} nH$$


From 1.13 式, leads R :

$$R_s = \frac{aR_{DC}}{2\delta} = \frac{l}{a} \sqrt{\frac{\mu_0 f}{\pi\sigma_{Cu}}} = 4.8\sqrt{f} \mu\Omega$$

From 1.16 式, leakage R :



$$R_e = \frac{1}{G_e} = \frac{\tan \Delta_s}{2\pi f C} = \frac{33.9 \times 10^6}{f} M\Omega$$
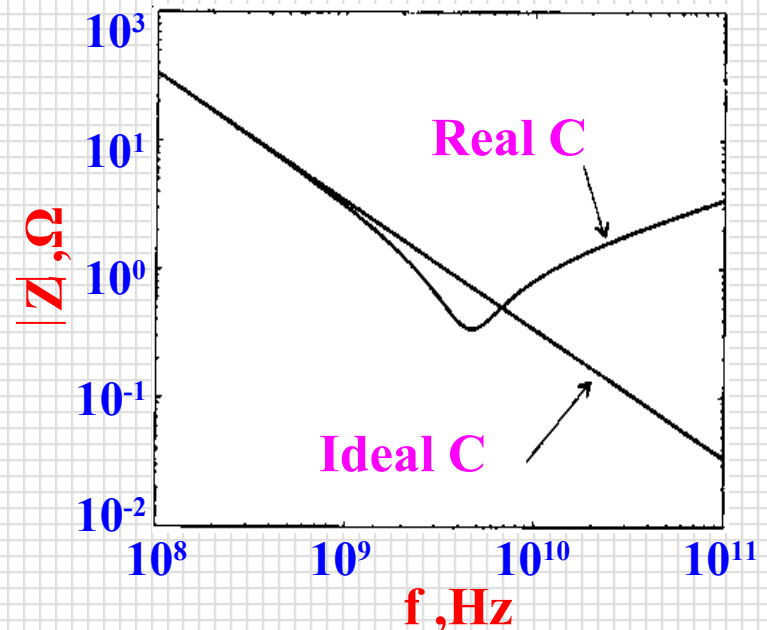
$$Z = j\omega L + R_s + \frac{1}{j\omega C + 1/R_e}$$



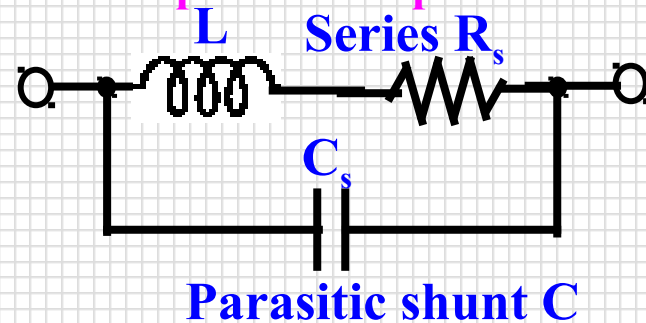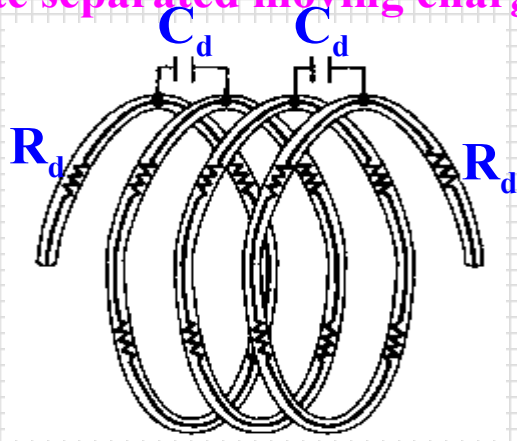1.4.3 High-frequency Inductors


Coil is formed by winding a wire on a cylindrical former, represent an inductance in addition to the frequency-dependent wire resistance. Adjacent wires constitute separated moving charges, giving rise to a parasitic capacitance effect.



Equivalent circuit inductor

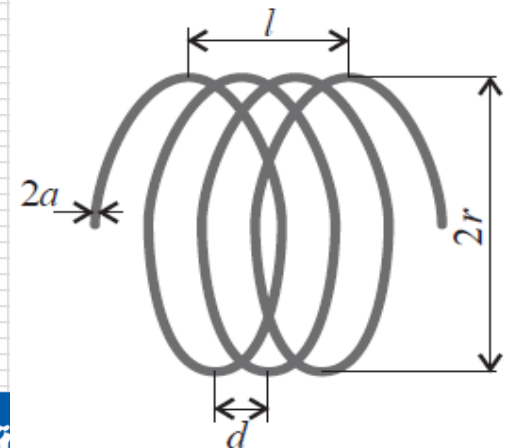Example 1.5 estimate the frequency response of an RFC formed by 3.5 turns of AWG36 copper wire on a 0.1 inch Air core. assume that the length of the coil is 0.05 inch

Solution : Table A.4 : AWG36 $a = 2.5\text{mil} = 63.5\mu$
 radius : $r = 50\text{mil} = 1.27\text{mm}$ (1inch=1000 mil)



Coil length : $l = 50\text{mil} = 1.27\text{mm}$

Distance between two turns :

$$d = l/N \approx 3.6 \times 10^{-4}\text{m}$$

Air core solenoid inductance :

$$L = \frac{\pi r^2 \mu_0 N^2}{l} = 61.4\text{nH}$$

from parallel-plate capacitor 1.14 ,


area $A = 2a l_{\text{wire}}$ ($= 2\pi r N$ length of wire) ,

$$\text{So equivalent C : } C_s = \frac{\epsilon A}{d} = \frac{\epsilon_0 \cdot 2\pi r N \cdot 2a}{l/N} = 4\pi\epsilon_0 \frac{raN^2}{l} = 0.087\text{pF}$$

$$\text{Neglect skin effect, series resistance : } R_s = \frac{l_{\text{wire}}}{\sigma_{\text{Cu}} \pi a^2} = \frac{2\pi r N}{\sigma_{\text{Cu}} \pi a^2} = 0.034\Omega$$

RFC find widespread use for biasing RF circuits , as tuning elements ,


$$\text{Quality factor : } Q = X / R_s$$

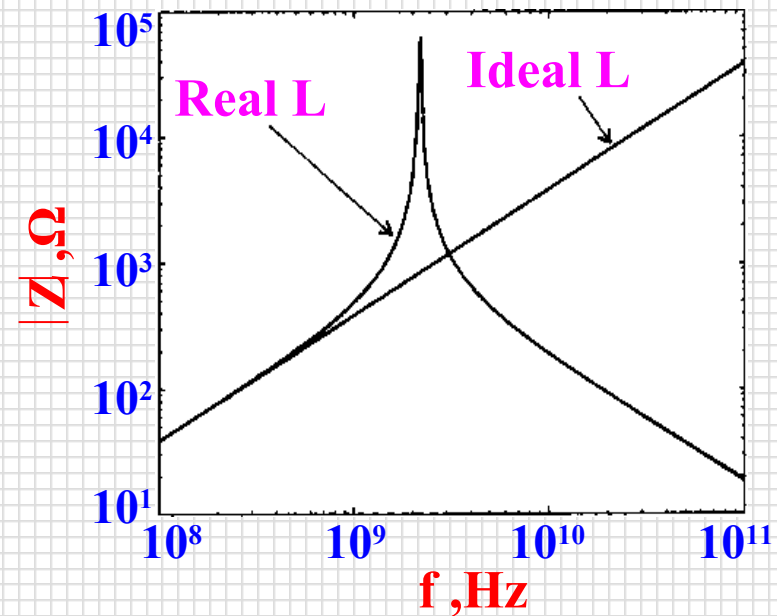


Easy welding

1.5 Chip components and circuit board considerations

1.5.1 chip resistors

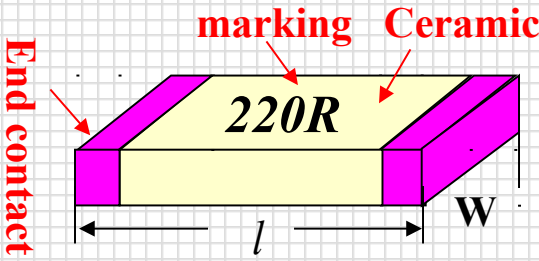geometry	Size code	Length(l) , mil	width(w) , mil
	0402	40	20
	0603	60	30
	0805	80	50
	1206	120	60
	1218	120	180


1.5.2 chip capacitors

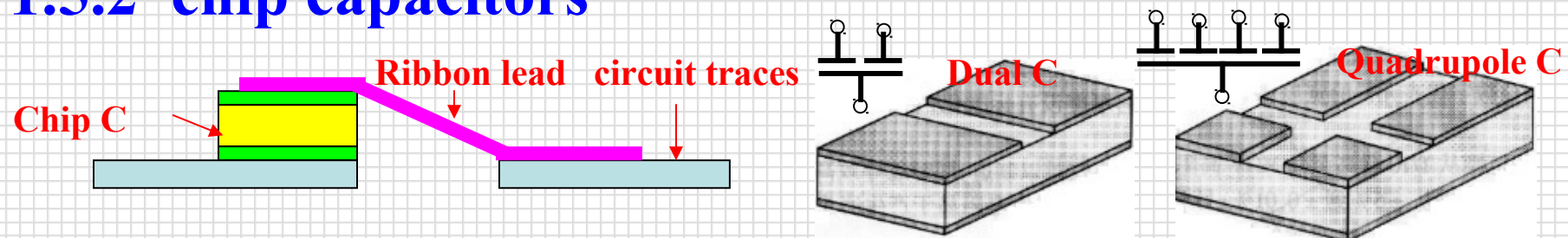

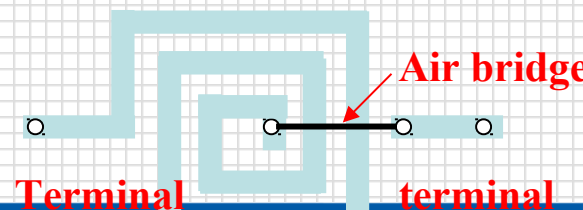1.5.3 surface-mounted Inductors

Still the wire-wound coil

Flat inductors can be integrated with microstrip



Summary

Electromagnetic wave nature begins to dominate over Kirch-hoff's current and voltage laws

Issues constant : $\beta = 2\pi / \lambda$, $v_p = \omega / \beta = 1 / \sqrt{\epsilon\mu}$



Consequence of the electromagnetic wave nature is skin effect : $\delta = 1 / \sqrt{\pi f \mu \sigma}$

Cylindrical lead wire : $R \approx R_{DC} \frac{a}{2\delta}$, $X = \omega L \approx R_{DC} \frac{a}{2\delta}$

These wires,in conjunction with the respective R C and L elements, form electric equivalent circuits whose performance deviate from the ideal element behavior
The physical dimensions of R C L are small ASAP , **when the wavelength is comparable in size with the discrete electronic components, basic circuit analysis no longer applies**

Exercise 1

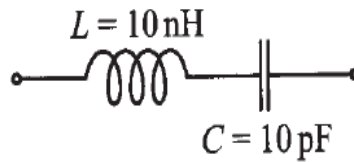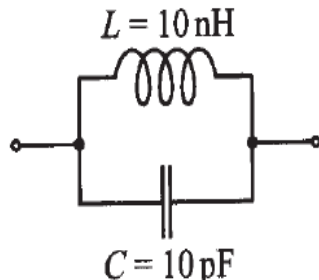- 1.1 Compute the phase velocity and wavelength in an FR4 printed circuit board whose relative dielectric constant is 4.6 and where the operational frequency is 1.92 GHz.
- 1.3 A coaxial cable that is assumed lossless has a wavelength of the electric and magnetic fields of $\lambda = 20$ cm at 960 MHz. Find the relative dielectric constant of the insulation
- 1.5 Find the frequency response of the impedance magnitude of the following series and parallel LC circuits:



- 1.10 The leads of a resistor in an RF circuit are treated as straight aluminum wires ($\sigma_{Al} = 4.0 \times 10^7$ S/m) of AWG size 14 and of total length of 5 cm. (a) Compute the DC resistance. (b) Find the AC resistance and inductance at 100 MHz, 1 GHz, and 10 GHz operating frequencies.

Chapter2 Transmission Line

Higher frequencies imply decreasing wavelengths , Voltages and currents no longer remain spatially uniform when compared to the geometric size of the discrete circuit elements , they have to be treated as propagating waves

2.1 why transmission line theory

assume the wave is confined to a conducting medium,

aligned with z-axis , E-field has a longitudinal component E_z

, give a voltage drop : $V = -\int E_z dl_z$

$E_x = E_{0x} \cos(\omega t - \beta z)$ in free space

Space characterized $\lambda = 2\pi/\beta$

Time period $T = 1/f$


assume $f = 1\text{MHz}$, $\epsilon_r = 10$, $\mu_r = 1$

From 2.1 , $v_p = \frac{\omega}{\beta} = \lambda f = \frac{1}{\sqrt{\epsilon_r \mu_r}} = \frac{c}{\sqrt{\epsilon_r \mu_r}}$

$\lambda = 94.86\text{m}$, for voltage wave :

$$V = -\int \cos(\omega t - \beta z) dz = \sin(\omega t - \beta z) / \beta$$

Spatially and temporally depicted

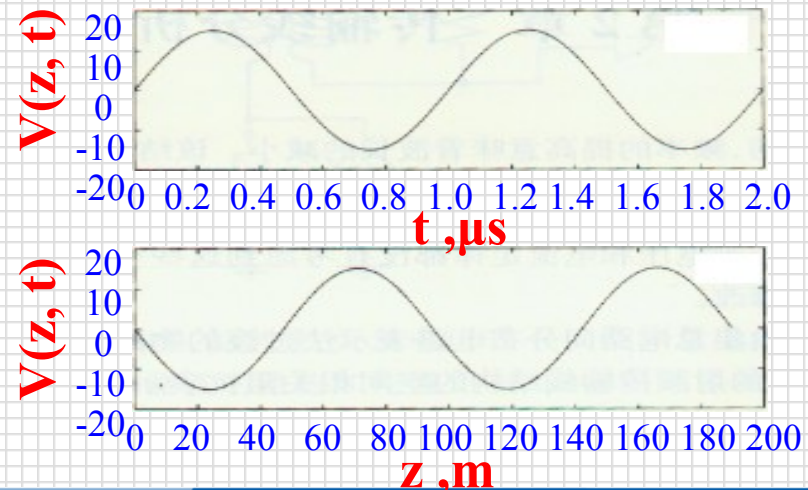

wire along z-zxis, length 1.5cm

resistance is negligible ,


$f=1\text{MHz}$ spatial voltage variations insignificant 。

$f=10\text{GHz}$, $\lambda =0.949\text{cm}$, same length , result as figure


Low-frequency, resistance negligible,

no patial voltage variation, use Kirchhoff's law

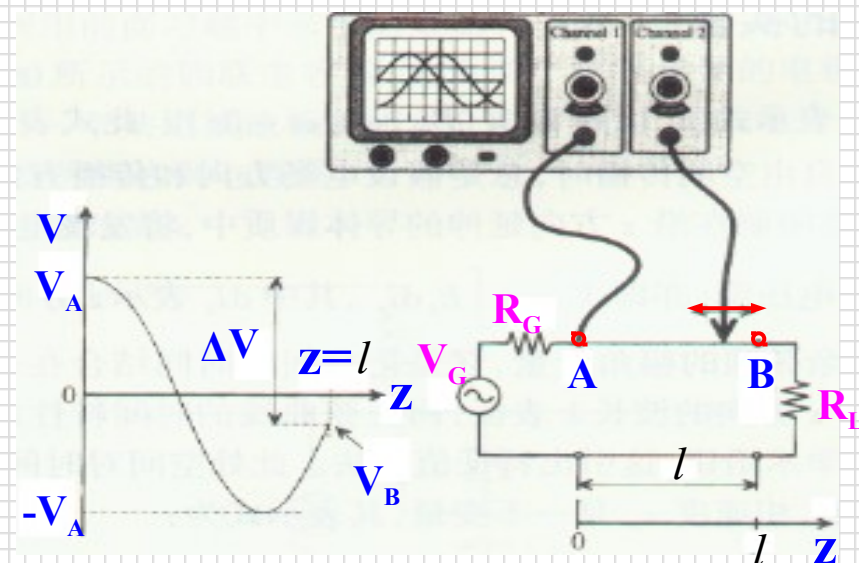High frequency, spatial behavior of Voltage and current , distributed Parameters R L C G (size more than a tenth of wavelength) 。




$$\sum_{i=1}^N V_i = 0$$

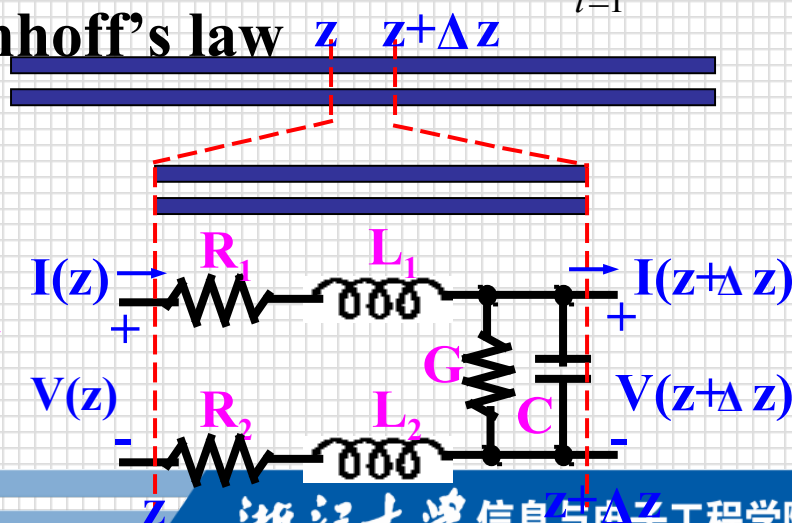


2.2 Transmission line


2.2.1 two-wire lines

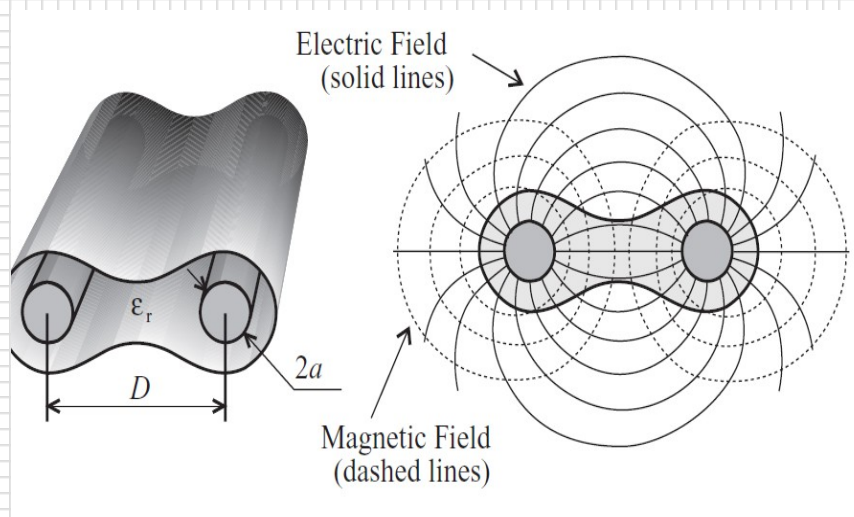


2.2.2 coaxial line

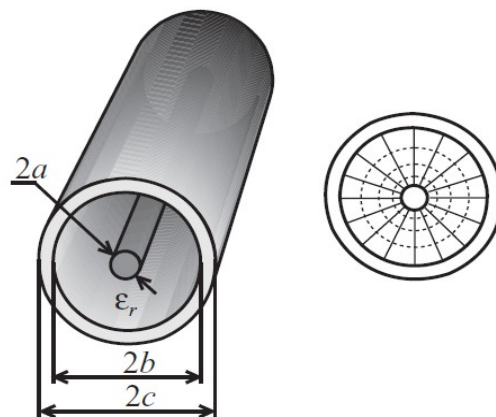



2.2.3 Microstrip

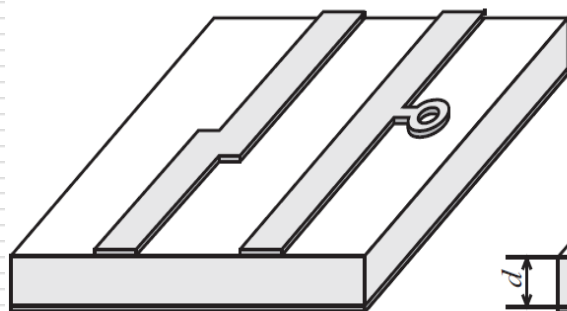


(a) Printed circuit board section

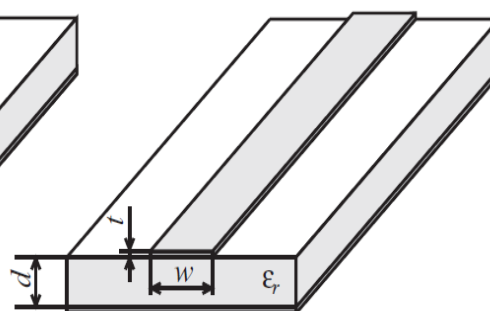


(b) Microstrip line

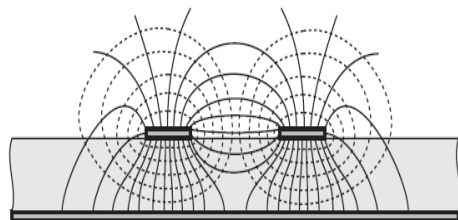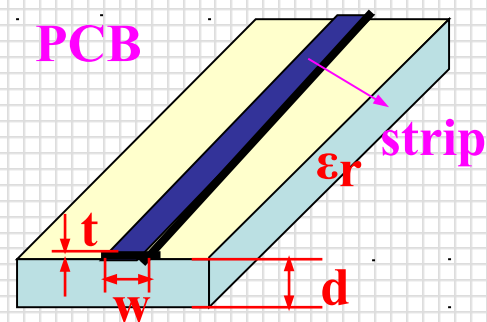


(a) Teflon epoxy ($\epsilon_r = 2.55$)

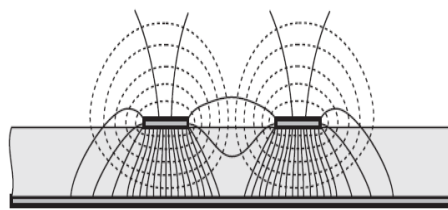


(b) Alumina ($\epsilon_r = 10.0$)

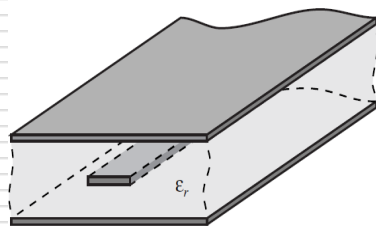

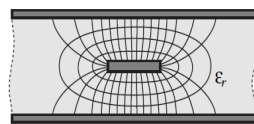
(a) Sandwich structure ($\epsilon_r = 2.55$)



(b) Cross-sectional field distribution

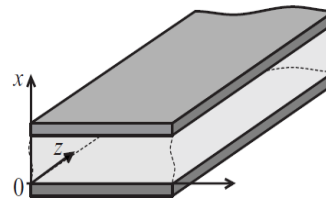

(a) Geometric representation

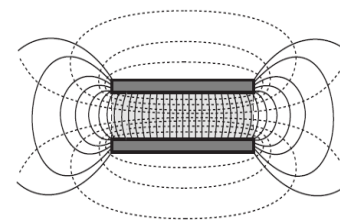

(b) Field distribution ($\epsilon_r = 2.55$)

2.3 equivalent circuit representation


On the geometric scale of RF circuit , voltage and currents are no longer spatially constant , Kirchhoff's laws cannot be applied over the macroscopic line Dimension. However, transmission line can be broken down into smaller segments , They are still large enough to contain all relevant electric characteristics, loss, inductive, capacitive effect. general equivalent circuit is shown in figure:

Advantage :

- Provides a clear intuitive physical picture
- lends itself to a standardized two-port network representation
- permits the analysis with Kirchhoff's laws
- provided building blocks that allow the expansion from microscopic to macroscopic forms

Disadvantage :

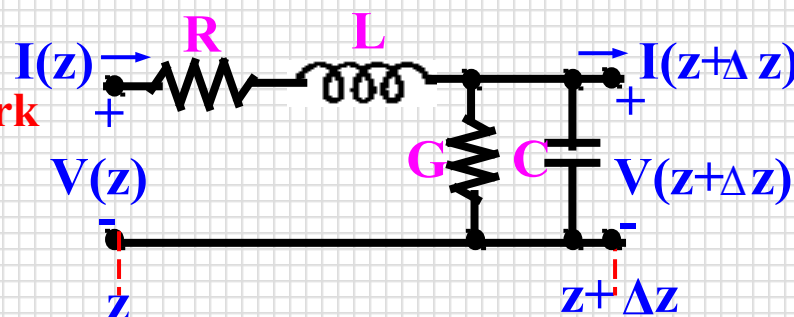- It is basically a one-dimensional analysis that does not take into account field fringing in the plane orthogonal to the direction of propagation and therefore can not predict interference with other components of the circuit ;
- Material-related nonlinearities due to hysteresis effects are neglected




2.6 Different line configurations

Parameter	Two-Wire Line	Coaxial Line	Parallel-Plate Line	Unit
R	$\frac{1}{\pi a \sigma_{\text{cond}} \delta}$	$\frac{1}{2\pi \sigma_{\text{cond}} \delta} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{2}{w \sigma_{\text{cond}} \delta}$	Ω/m
L	$\frac{\mu}{\pi} \text{acosh}\left(\frac{D}{2a}\right)$	$\frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)$	$\mu \frac{d}{w}$	H/m
G	$\frac{\pi \sigma_{\text{diel}}}{\text{acosh}(D/(2a))}$	$\frac{2\pi \sigma_{\text{diel}}}{\ln(b/a)}$	$\sigma_{\text{diel}} \frac{w}{d}$	S/m
C	$\frac{\pi \epsilon}{\text{acosh}(D/(2a))}$	$\frac{2\pi \epsilon}{\ln(b/a)}$	$\epsilon \frac{w}{d}$	F/m

2.7 Transmission line equation

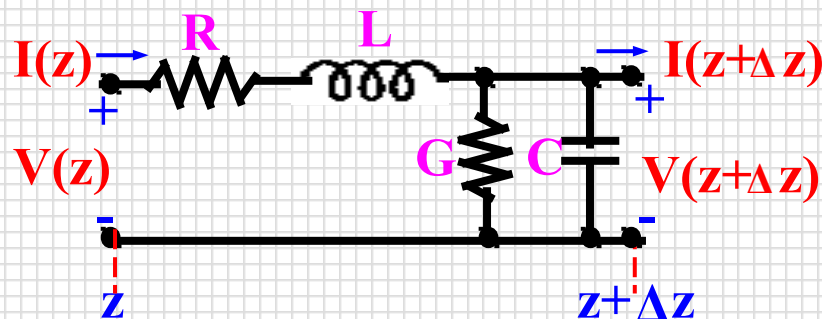2.7.1 Kirchhoff voltage and current law representations



Use KVL : $(R + j\omega L)I(z)\Delta z + V(z + \Delta z) = V(z)$ (2.26)

Differential : $\lim_{\Delta z \rightarrow 0} \left(-\frac{V(z + \Delta z) - V(z)}{\Delta z} \right) = -\frac{dV(z)}{dz} = (R + j\omega L)I(z)$ (2.28)

From KCL : $I(z) - V(z + \Delta z)(G + j\omega C)\Delta z = I(z + \Delta z)$ (2.29)

Differential : $\lim_{\Delta z \rightarrow 0} \frac{I(z + \Delta z) - I(z)}{\Delta z} = \frac{dI(z)}{dz} = -(G + j\omega C)V(z)$ (2.30)

2.7.2 Traveling voltage and current waves

$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z) \quad \frac{dI(z)}{dz} = -(G + j\omega C)V(z) \quad \text{differentiating}$$

$$\text{Obtain: } \frac{d^2V(z)}{dz^2} - k^2V(z) = 0 \quad \frac{d^2I(z)}{dz^2} - k^2I(z) = 0$$

$$\text{where } k = k_r + jk_i = \sqrt{(R + j\omega L)(G + j\omega C)} \quad \text{complex propagation constant (2.32)}$$

$$\text{Solution } V(z) = V^+e^{-kz} + V^-e^{kz}, \quad I(z) = I^+e^{-kz} + I^-e^{kz}$$

+ +z-direction
- -z-direction

2.7.3 General Impedance definition

$$\text{substituted } V(z) = V^+e^{-kz} + V^-e^{kz} \text{ into } -\frac{dV(z)}{dz} = (R + j\omega L)I(z) \quad \text{differentiationg}$$

$$: \quad I(z) = k(V^+e^{-kz} - V^-e^{kz}) / (R + j\omega L)$$

Characteristic impedance :

$$Z_0 = \frac{R + j\omega L}{k} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (2.37)$$

$$I(z) = \frac{k}{R + j\omega L} (V^+ e^{-kz} - V^- e^{kz}) = I^+ e^{-kz} + I^- e^{kz} \quad \text{so : } Z_0 = \frac{V^+}{I^+} = \frac{V^-}{I^-}$$

2.7.4 Lossless transmission line model

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu}{\varepsilon}} \frac{d}{w} \quad (2.41)$$

lossless : $R=G=0$

L and C given in Table 2.1

2.8 Microstrip transmission lines

Substrate thickness increases or conductor width decreases, fringing fields become more prominent and cannot be ignored in the mathematical models. Aliens have developed approximate expressions for calculation of the characteristic line impedance, taking into account conductor width and thickness. (when : conductor thickness/substrate height= $t/h < 0.005$).

when $w/h < 1$:
$$Z_0 = \frac{Z_f}{2\pi\sqrt{\epsilon_{eff}}} \ln\left(\frac{8h}{w} + \frac{w}{4h}\right)$$
 Empirical formulas

Wave impedance in free space $Z_f = \sqrt{\mu_0\epsilon_0} = 376.8\Omega$



Effective dielectric constant

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[\left(1 + 12\frac{h}{w}\right)^{-1/2} + 0.04\left(1 - \frac{w}{h}\right)^2 \right]$$

when $w/h > 1$

$$Z_0 = \frac{Z_f}{\sqrt{\epsilon_{eff} \left(1.393 + \frac{w}{h} + \frac{2}{3} \ln \left(\frac{w}{h} + 1.444 \right) \right)}}$$
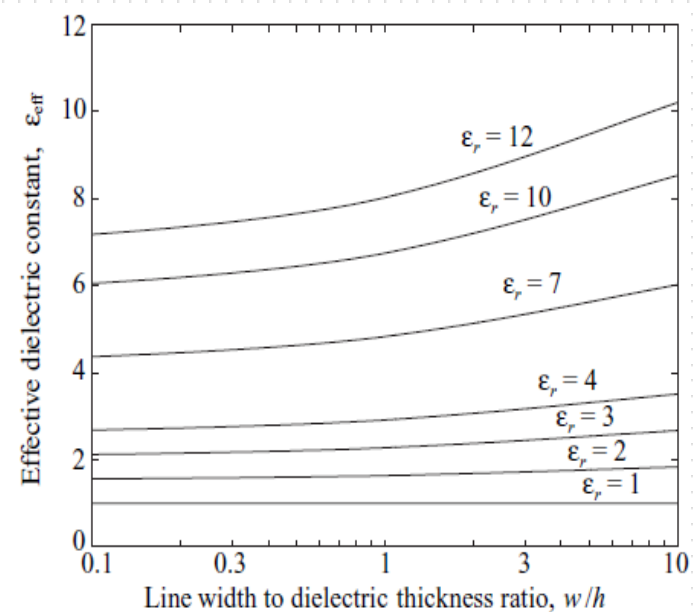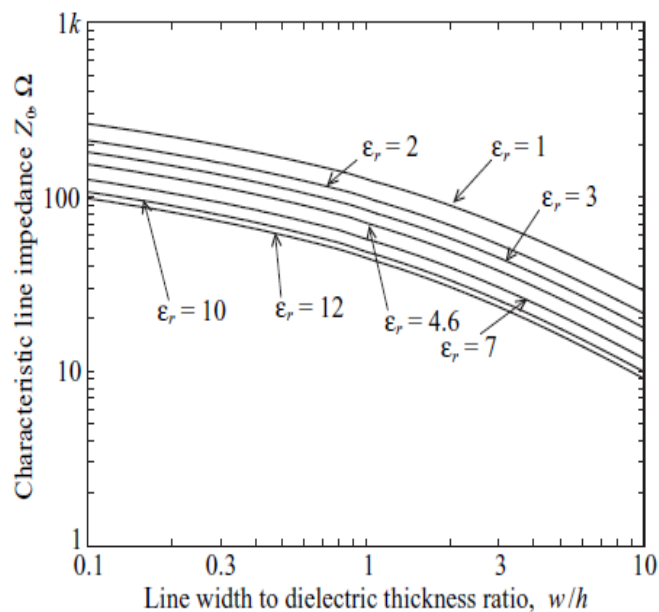
$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + 12 \frac{h}{w} \right)^{-1/2}$$



Get w/h ratios based on a given characteristic impedance

when $w/h \leq 2$ $\frac{w}{h} = \frac{8e^A}{e^{2A} - 2}$

when $w/h \geq 2$ $\frac{w}{h} = \frac{2}{\pi} \left\{ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left[\ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right] \right\}$

where $A = 2\pi \frac{Z_0}{Z_f} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.23 + \frac{0.11}{\epsilon_r} \right)$, $B = \frac{\pi Z_f}{2Z_0 \sqrt{\epsilon_r}}$

Example 2.5 line impedance $Z_0=50\Omega$, selected FR-4 PCB, with $\epsilon_r=4.6$, $h=40$ mil, What are the width of the trace, phase velocity and wavelength at 2GHz

Solution : Use Figure 2.20 $\epsilon_r=4.6$, $Z_0=50\Omega$ determine $w/h=1.9$.

$$A = 2\pi \frac{Z_0}{Z_f} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.23 + \frac{0.11}{\epsilon_r} \right) = 1.5583$$

$$w/h = 8e^A / (e^{2A} - 2) = 1.8477$$

$$w = 1.8477 \times 40 = 73.9 \text{ mil}$$

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + 12 \frac{h}{w} \right)^{-1/2} = 3.4575$$

$$v_p = c / \sqrt{\epsilon_{eff}} = 1.61 \times 10^8 \text{ m/s}, \quad \lambda = v_p / f = 80.67 \text{ mm}$$

The assumption of zero thickness of the strip line may not be valid and corrections to be preceding equations are needed.

Effective width :

$$w_{eff} = w + \frac{t}{\pi} \left(1 + \ln \frac{2x}{t} \right)$$

when $w > h / 2\pi > 2t, \quad x = h$


when $h / 2\pi > w > 2t, \quad x = 2\pi w$

2.9 Terminated lossless transmission line

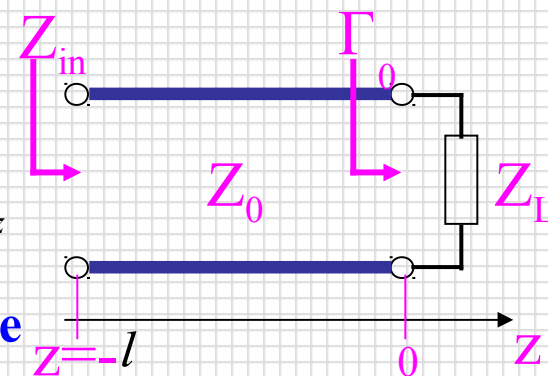2.9.1 Voltage reflection coefficient

The load is located at $z=0$, the voltage wave is coupled into the line at $z=-l$.

So the voltage anywhere along the line: $V(z) = V^+ e^{-kz} + V^- e^{kz}$



Reflection coefficient : $\Gamma_0 = \frac{V^-}{V^+}$ **Reflected voltage wave**
Incident voltage wave

$$\text{At } z=0 : \quad V(z) = V^+ (e^{-kz} + \Gamma_0 e^{kz}), \quad I(z) = \frac{V^+}{Z_0} (e^{-kz} - \Gamma_0 e^{kz})$$

$$\text{then : } Z(0) = Z_L = \frac{V(0)}{I(0)} = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0} \quad \text{So : } \Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (2.52)$$

when $Z_L \rightarrow \infty$ **open line** $\Gamma_0 = 1$, **reflected and incident wave the same ploarity**

when $Z_L = 0$ **short** $\Gamma_0 = -1$, **reflected wave inverted amplitude**

When $Z_L = Z_0$ **match** $\Gamma_0 = 0$, **no reflection, abosorbed by the load**

2.9.2 Propagation Constant and Phase Velocity

Complex propagation constant : $k = k_r + jk_i = \sqrt{(R + j\omega L)(G + j\omega C)}$

For lossless line : $k = j\omega\sqrt{LC}$

Engineering notation : $\alpha \equiv k_r = 0$

$$\beta \equiv k_i = \omega\sqrt{LC}$$

Then : $V(z) = V^+ (e^{-j\beta z} + \Gamma_0 e^{j\beta z})$,

Attenuation coefficient

**Wave number or
propagation constant**

$$I(z) = \frac{V^+}{Z_0} (e^{-j\beta z} - \Gamma_0 e^{j\beta z}) \quad (2.56)$$

(2.57)

1.3 :

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

independent with frequency

Dispersion-free transmission . In reality we have to take into account a certain Degree of frequency dependence or dispersion of the phase velocity that causes Signal distortion

2.9.3 standing waves



Insert the reflection coefficient for a short-circuit line into 2.56
change to a new coordinate d :

$$V(d) = V^+ (e^{j\beta d} - e^{-j\beta d})$$

Phase expression to time domain : $e^{j\beta d} - e^{-j\beta d} = 2j \sin(\beta d)$

$$\begin{aligned} v(d, t) &= \text{Re}\{V e^{j\omega t}\} \\ &= \text{Re}\{2jV^+ \sin(\beta d) e^{j\omega t}\} \\ &= -2V^+ \sin(\beta d) \sin\omega t \end{aligned}$$

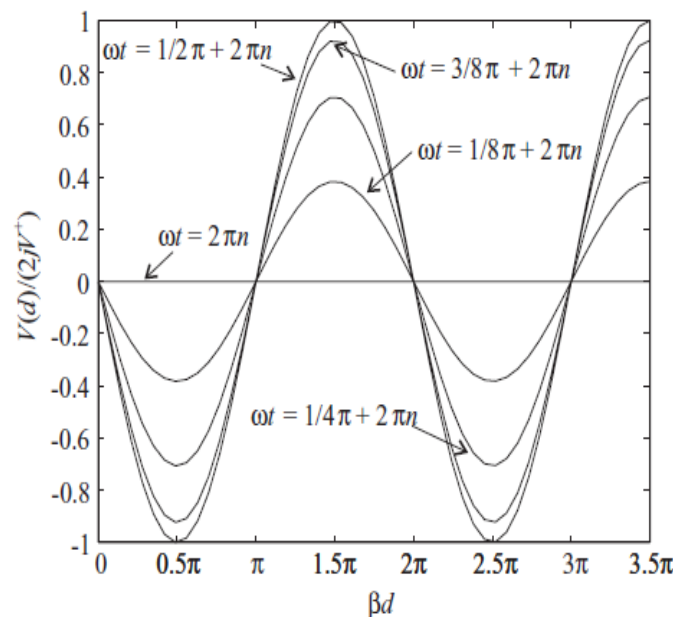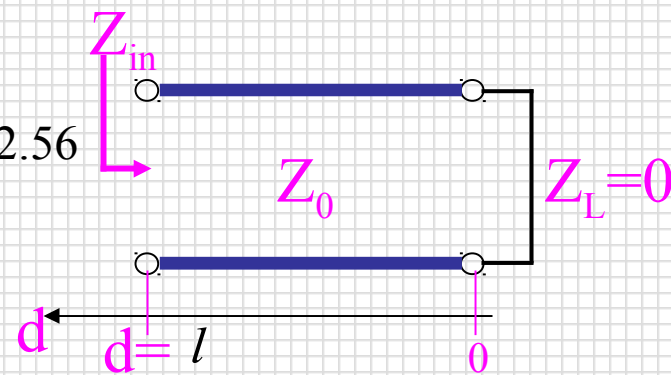$\sin(\beta d)$ for $d=0$ voltage maintains the
Short condition at all time instance t .
The incident wave is 180° out of phase
Fixed zero crossing at $0, \lambda/2, \lambda, 3\lambda/2, \dots$



Voltage : $V(d) = V^+ e^{j\beta d} (1 + \Gamma_0 e^{-j2\beta d}) = A(d)[1 + \Gamma(d)]$

Current : $I(d) = \frac{V^+}{Z_0} e^{j\beta d} (1 - \Gamma_0 e^{-j2\beta d}) = \frac{A(d)}{Z_0} [1 - \Gamma(d)]$

Reflection coefficient : $\Gamma(d) = \Gamma_0 e^{-j2\beta d} \quad (2.64)$

Matched condition , $\Gamma_0 = 0$, $\Gamma(d) = 0$, maintaining propagation wave

Standing wave ratio : $SWR = \frac{|V_{\max}|}{|V_{\min}|} = \frac{|I_{\max}|}{|I_{\min}|} = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|}$

Extreme values of (2.64) can only be +1 and -1

match termination $SWR=1$, open or short $SWR \rightarrow \infty$

Strictly speaking, SWR can only be applied to lossless lines. The magnitude of The voltage or current waves diminishes as a function of distance due to attenuation . Because most RF systems possess very low losses, SWR can be Safely applied.

2.10 Special termination Condition

2.10.1 Input impedance of terminated lossless line

Distance d from the load, the impedance :

$$Z_{in}(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)} = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)}$$

$$\begin{aligned} V(d) &= A(d)[1 + \Gamma(d)] \\ I(d) &= \frac{A(d)}{Z_0}[1 - \Gamma(d)] \\ \Gamma(d) &= \Gamma_0 e^{-j2\beta d} \\ \Gamma_0 &= \frac{Z_L - Z_0}{Z_L + Z_0} \end{aligned}$$

Predict how the load impedance Z_L is transformed along a transmission line of Characteristic impedance Z_0 and length d .

2.10.2 Short Circuit transmission line

$$Z_L = 0 : \quad Z_{in}(d) = jZ_0 \tan(\beta d)$$

$d=0$, $Z_{in}(d) = Z_L = 0$; increasing d ,


the impedance is increase and inductive behavior

$d=\lambda/4$, $Z_{in}(d)=\infty$, open-circuit condition ;

Further increase , negative imaginary impedance

Capacitive behavior

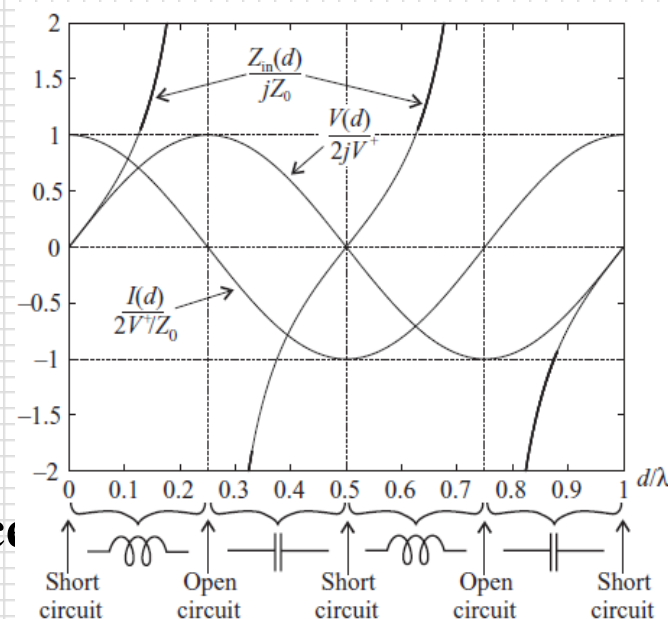$d=\lambda/2$, $Z_{in}(d)=0$, entire periodic repeated




2.10.3 Open-circuit transmission line

$$\text{If } Z_L \rightarrow \infty : \quad Z_{in}(d) = \frac{-jZ_0}{\tan(\beta d)}$$

Keep the length d fixed, sweep the frequency over a specified range


2.10.4 Quarter-wave transmission line

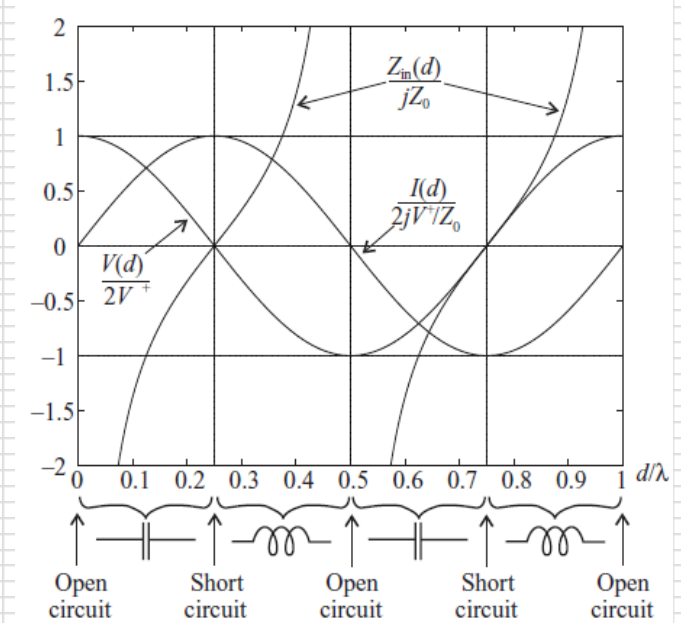

If $Z_L = Z_0$: $Z_{in}(d) = Z_0$ regardless length

If $d = \lambda/2$: $Z_{in}(d) = Z_L$ independent with Z_0

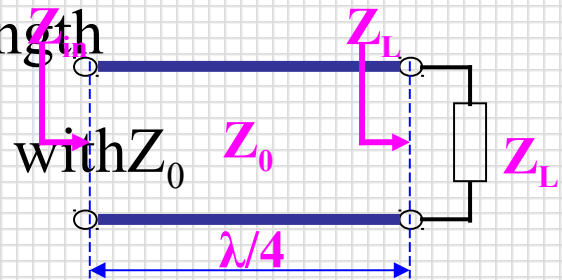And : $Z_{in}(d = \lambda/4) = Z_0^2 / Z_L$




Lambda-quarter transformer , matching of a real load impedance to a desired Real input impedance by choosing a segment : $Z_0 = \sqrt{Z_L Z_{in}}$ (2.82)

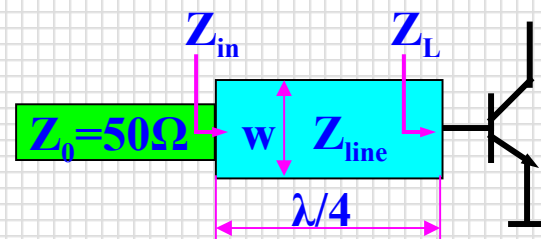Example 2.8 A transistor input impedance 25Ω , at 500MHz matched to a 50Ω microstrip line . Thickness of dielectric 1mm, $\epsilon_r = 4$, loss is neglected , Find the length, width and characteristic impedance of $\lambda/4$ parallel-plate line Transformer for which matching is achieved .

Solution : $Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu}{\epsilon}} \frac{d}{w}$ $Z_0 = \sqrt{Z_L Z_{in}}$

Line impedance : $Z_{line} = \sqrt{Z_{in} Z_L} = 35.355\Omega = \sqrt{\mu / \epsilon d / w}$




Then : $w = \sqrt{\mu_0 / \epsilon_0 \epsilon_r d / Z_{line}} = 5.239 \text{ mm}$

$L = \mu d / w = 235.8 \text{ nH / m}, \quad C = \epsilon w / d = 188.6 \text{ pF / m}$

$l = \frac{\lambda}{4} = \frac{v_p}{4f} = \frac{1}{4f\sqrt{LC}} = 74.967 \text{ mm}$

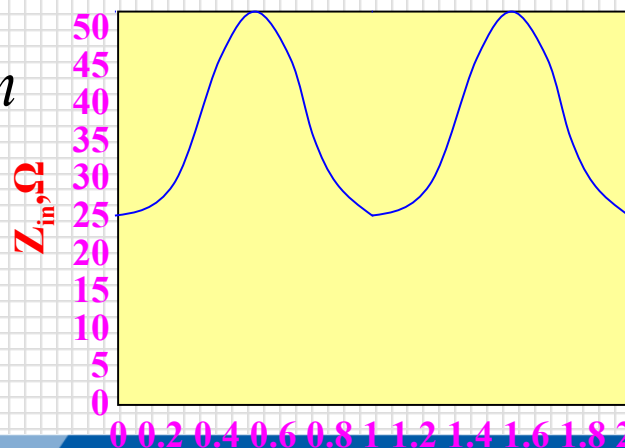From : $Z_{in}(d) = Z_{line} \frac{1 + \Gamma_0 e^{-j2\beta d}}{1 - \Gamma_0 e^{-j2\beta d}}$ Get figure




matched not only at 500MHz, but also 1.5 GHz
Cannot work over a wide frequency band

2.11 Sourced and loaded transmission line

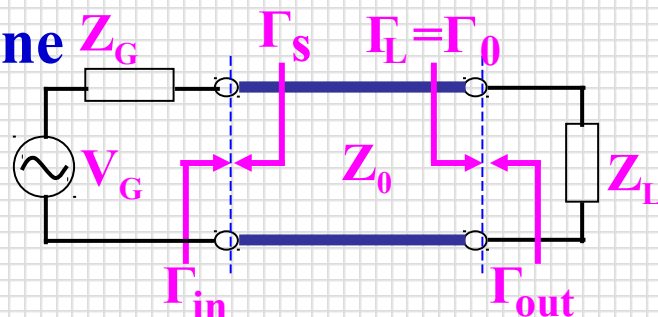2.11.1 Phasor representation of source

Input voltage at the beginning of the transmission line :

$$V_{in} = V_{in}^+ + V_{in}^- = V_{in}^+ (1 + \Gamma_{in}) = V_G \frac{Z_{in}}{Z_{in} + Z_G}$$



仿照 $\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$ 得出

from $\Gamma(d) = \Gamma_0 e^{-j2\beta d}$, input reflection : $\Gamma_{in} = \Gamma(d=l) = \Gamma_0 e^{-j2\beta l} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$

Transmission coefficient :

$$T_{in} = 1 + \Gamma_{in} = \frac{2Z_{in}}{Z_{in} + Z_0}, \quad T_0 = 1 + \Gamma_0 = \frac{2Z_L}{Z_L + Z_0} \text{ example 2.9}$$

The connected source introduces an additional difficulty. Since the voltage reflected from the Load is traveling toward the source, we need to consider a mismatch between the transmission Line and the source impedance .

The source reflection coefficient : $\Gamma_s = \frac{Z_G - Z_0}{Z_G + Z_0}$

And : $\Gamma_{out} = \Gamma_s e^{-j2\beta l}$

2.11.2 Power considerations for a transmission line

Voltage : $V_{in} = V_{in}^+ (1 + \Gamma_{in})$
 Current : $I_{in} = V_{in}^+ (1 - \Gamma_{in}) / Z_0$

Time-averaged power :

$$P_{in} = P_{in}^+ + p_{in}^- = \frac{1}{2} \operatorname{Re}\{VI^*\} = \frac{1}{2} \frac{|V_{in}^+|^2}{Z_0} (1 - |\Gamma_{in}|^2)$$

2.69 :

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}$$

$$Z_G = Z_0 \frac{1 + \Gamma_S}{1 - \Gamma_S}$$

Then :
$$V_{in}^+ = \frac{V_{in}}{1 + \Gamma_{in}} = \frac{V_G}{1 + \Gamma_{in}} \frac{Z_{in}}{Z_{in} + Z_G} = \frac{V_G}{2} \frac{1 - \Gamma_S}{1 - \Gamma_S \Gamma_{in}}$$

$$P_{in} = \frac{1}{8} \frac{|V_G|^2}{Z_0} \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \Gamma_0 e^{-j2\beta l}|^2} \left(1 - |\Gamma_0 e^{-j2\beta l}|^2 \right)$$

$$|V_L^+| = |V_{in}^+| e^{-\alpha l}$$

a attenuation coefficient


Lossless line and matched :

$$P_{in} = \frac{1}{8} \frac{|V_G|^2}{Z_0} = \frac{1}{8} \frac{|V_G|^2}{Z_G}$$

Lossy line :
$$P_L = \frac{|V_L^+|^2}{2Z_0} (1 - |\Gamma_L|^2) = \frac{1}{8} \frac{|V_G|^2}{Z_0} \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \Gamma_{in}|^2} (1 - |\Gamma_L|^2) e^{-2\alpha l}$$

2.11.3 Input impedance matching

$$P_{in} = \frac{1}{2} \operatorname{Re} \left\{ V_{in} \frac{V_{in}^*}{Z_{in}^*} \right\} = \frac{1}{2} \frac{|V_G|^2}{\operatorname{Re} \{ Z_{in}^* \}} \left| \frac{Z_{in}}{Z_G + Z_{in}} \right|^2$$

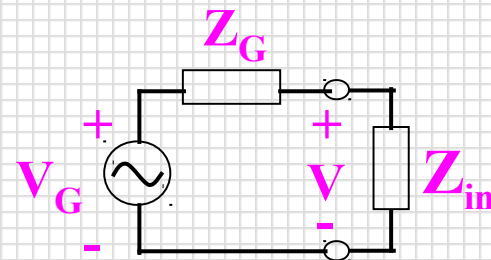

Maximum power value : $\frac{\partial P_{in}}{\partial R_{in}} = \frac{\partial P_{in}}{\partial X_{in}} = 0$

$$Z_{in} = Z_G^*$$

$$Z_{out} = Z_L^*$$

2.11.4 Return loss and insertion loss

Practical circuit suffer a degree of mismatch Γ_{in} is not zero

Return Loss : $RL = -10 \log \frac{P_r (= P_{in}^-)}{P_i (= P_{in}^+)} = -10 \log |\Gamma_{in}|^2 = -20 \log |\Gamma_{in}| = -\ln |\Gamma_{in}|$
Reflected power
Incident power Decibel(dB) Nepers(N)

In addition to the return loss, also introduce insertion loss

Insertion Loss : $IL = -10 \log \frac{P_t}{P_i} = -10 \log \frac{P_i - P_r}{P_i} = -10 \log (1 - |\Gamma_{in}|^2)$
Transmitted power
Incident power