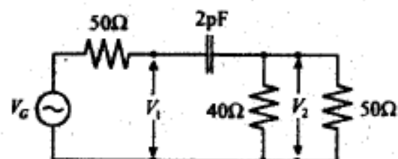


## homework 5

For the simple integrator circuit shown,



determine the following quantities:

- Transfer function  $H(\omega) = V_2/V_G$
- Attenuation versus frequency behavior  $\alpha(\omega)$
- Phase versus frequency behavior  $\phi(\omega)$
- Group delay  $t_g$

Plot these factors for the frequency range from DC to 1 GHz.

For the simple integrator circuit shown,

Determine the following quantities:

- 1 Transfer function  $H(\omega)=V_2/V_G$
- 2 Attenuation versus frequency behavior  $\alpha(\omega)$
- 3 Phase versus frequency behavior  $\phi(\omega)$
- 4 Group delay  $t_g$

Plot these factors for the frequency range from DC to 1GHz.

假设电阻从左到右依次为  $R_1, R_2, R_3$ 。则可以得到如下的矩阵模式:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & R_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{j\omega C} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{R_2} & 1 \end{bmatrix}, \begin{bmatrix} 1 & 0 \\ \frac{1}{R_3} & 1 \end{bmatrix} = \begin{bmatrix} 1 + (\frac{1}{j\omega C} + R_1)(\frac{1}{R_2} + \frac{1}{R_3}) & \frac{1}{j\omega C} + R_1 \\ \frac{1}{R_2} + \frac{1}{R_3} & 1 \end{bmatrix}$$

所以, 可以得到传输函数:

$$H(\omega) = \frac{1}{A} = \frac{1}{1 + (\frac{1}{j\omega C} + R_1)(\frac{1}{R_2} + \frac{1}{R_3})}$$

其图像为:

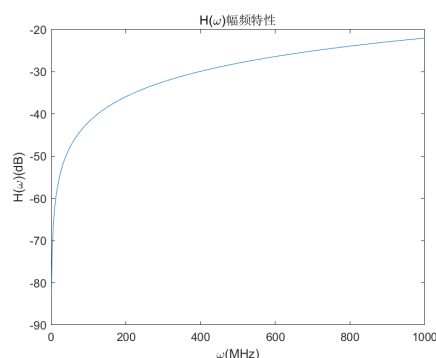


Figure 1: transfer function

Attenuation factor:

$$\alpha(\omega) = -\ln(|H(\omega)|) = -20\log(|H(\omega)|)$$

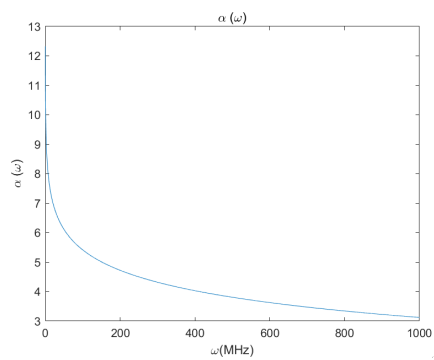


Figure 2: Attenuation factor

Corresponding phase:

$$\phi(\omega) = \arctan\left(\frac{\text{Im}(H(\omega))}{\text{Re}(H(\omega))}\right)$$

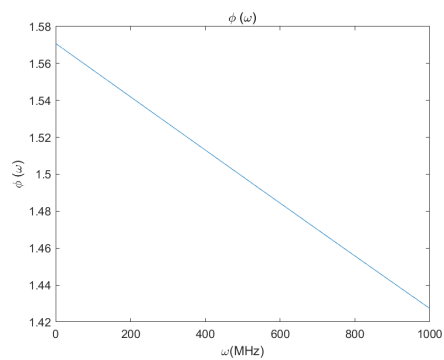


Figure 3: Corresponding phase

Group delay:

$$t_g = \frac{d\phi(\omega)}{d\omega}$$

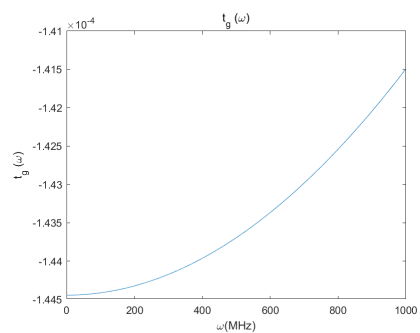


Figure 4: Group delay

matlab 代码附下:

```
1 %已知参数
2 omega=0:0.1:1000;
3 omega_g=omega.*10^6;
4 r1=50;
5 r2=40;
6 r3=50;
7 c=2e-12;
8
9 %transfer function
10 H=1./(1+(1./(1i.*omega_g.*c)+r1).*(1/r2+1/r3));
11 Hr=10*log10(real(H));
12 figure(1);
13 plot(omega,Hr);
14 title("H(\omega) 幅频特性");
15 xlabel("\omega(MHz)");
16 ylabel("H(\omega)(dB)");
17
18 %Attenuation factor
19 a=-log(abs(H));
20 figure(2);
21 plot(omega,a);
22 title("\alpha (\omega)");
23 xlabel("\omega(MHz)");
24 ylabel("\alpha (\omega)");
25
26 %Corresponding phase
27 phi=atan(imag(H)./real(H));
28 figure(3);
29 plot(omega,phi);
30 title("\phi (\omega)");
31 xlabel("\omega(MHz)");
32 ylabel("\phi (\omega)");
33
34 %Group delay
35 aphi=diff(phi);
36 aw=diff(omega);
37 tg=aphi./aw;
38 figure(4);
39 plot(omega(1:end-1),tg);
40 title("t_g (\omega)");
41 xlabel("\omega(MHz)");
42 ylabel("t_g (\omega)");
```