

## 第二章 动态电路瞬态特性分析

### 2.5 RC电路充放电

# RC电路充放电

- RC电路充电
- RC电路放电
- RC电路充放电仿真

# RC电路的充电


阶跃电压激励  $v_i(t) = V_s \cdot u(t) = \begin{cases} 0 & t < 0 \\ V_s & t > 0 \end{cases}$

围绕节点①列写KCL方程

$$C \frac{dv_c(t)}{dt} + \frac{v_c(t) - v_i(t)}{R} = 0$$

$$CsV_c(s) + \frac{V_c(s) - V_s/s}{R} = 0 \rightarrow RCsV_c(s) + V_c(s) - V_s/s = 0$$

$$V_c(s) = \frac{V_s}{s(1 + sRC)}$$

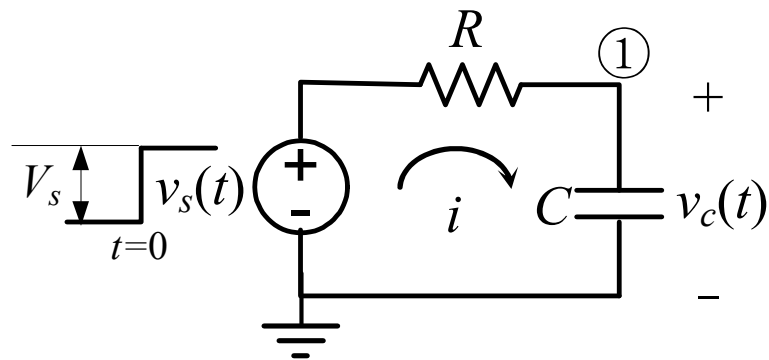

设  $v_c(0)=0$

# RC电路的充电

$$V_c(s) = \frac{V_s}{s(1 + sRC)}$$

```
syms RC Vs s;
```

```
VS=Vs/s/(1+s*RC)
```

```
Vt=ilaplace(VS)
```

```
VS =
```

```
Vs/(s*(RC*s + 1))
```

```
Vt =
```

```
Vs - Vs*exp(-t/RC)
```

```
>>
```


$$V_c(t) = V_s \left( 1 - e^{-\frac{t}{RC}} \right) = V_s \left( 1 - e^{-\frac{t}{\tau}} \right), \quad \tau = RC$$

# RC电路的充电

$$V_c(t)|_{V_s=1, RC=1} = 1 - e^{-t}$$

- $V_s=1$  (单位阶跃电压)
- $RC=1$  (归一化)
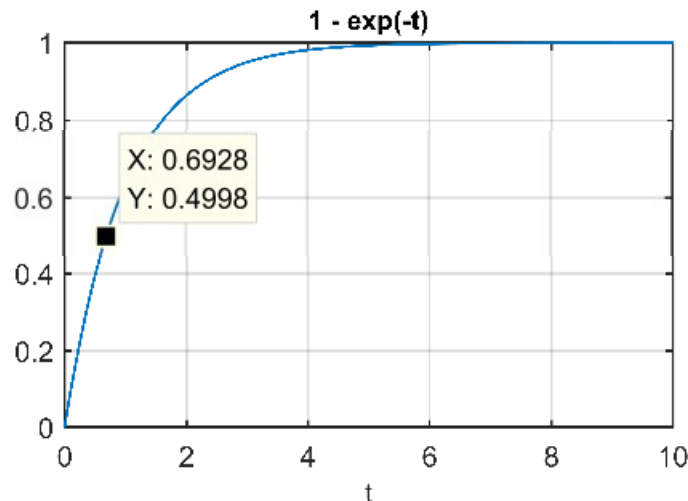
`ezplot(Vt, [0, 10]);ylim([0 1]);grid on;`



电容器电压达到一个特定值  $v_c(t_x) = V_x$  所需时间


$$t_x = \ln\left(\frac{1}{1 - V_x}\right)$$

$$0.5 = 1 - e^{-t_{50\%}} \rightarrow t_{50\%} = \ln\left(\frac{1}{1 - 0.5}\right) = 0.7$$
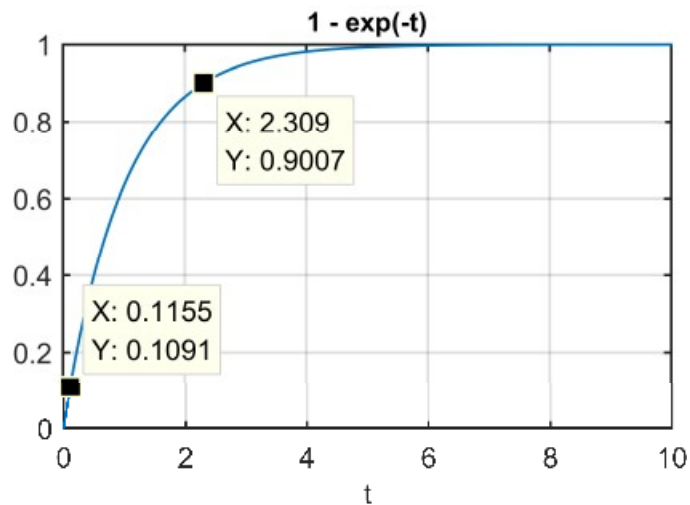
# RC电路的充电

充电过程中电容器电压上升时间  
 $t_{LH}$  定义为

$$t_{LH} = t_{90\%} - t_{10\%} = \ln\left(\frac{1}{1-0.9}\right) - \ln\left(\frac{1}{1-0.1}\right) = 2.2$$




$$t_{LH} = 2.309 - 0.1155 = 2.19$$

# RC电路的放电

电源短路，电容初始储能不为零

$$v_c(0^-) = V_s \neq 0$$

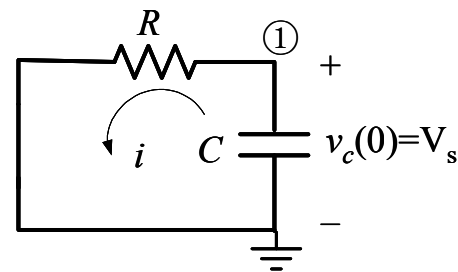

$$\frac{v_c(t)}{R} + C \frac{dv_c(t)}{dt} = 0$$

$$f(t) \leftrightarrow F(s)$$

$$\frac{d}{dt} f(t) = sF(s) - f(0^-)$$

$$\frac{V_c(s)}{R} + C(sV_c(s) - v_c(0^-)) = 0, v_c(0^-) = V_s$$

$$V_c(s) = \frac{V_s}{s + \frac{1}{RC}}$$

# RC电路的放电

$$V_c(s) = \frac{V_s}{s + \frac{1}{RC}}$$

`syms RC Vs s;`

`VS=Vs/(s+1/(RC))`

`Vt=ilaplace(VS)`

`VS =`

`Vs/(s + 1/RC)`

`Vt =`

`Vs*exp(-t/RC)`

`>>`

$$v_c(t) = V_s e^{-\frac{t}{RC}} = V_s e^{-\frac{t}{\tau}}, \tau = RC$$



# RC电路的放电

$$V_c(t)|_{V_s=1, RC=1} = e^{-t}$$

$V_s=1$  (单位阶跃电压)

$RC=1$  (归一化)


```
ezplot(Vt, [0, 10]);ylim([0 1]);grid on;
```

$$0.5 = e^{-t_{50\%}} \rightarrow t_{50\%} = \ln \frac{1}{0.5} = 0.7$$

$$t_{HL} = t_{10\%} - t_{90\%} = \ln\left(\frac{1}{0.1}\right) - \ln\left(\frac{1}{0.9}\right) = 2.2$$

放电过程中电容器电压下降


时间 $t_{HL}$   $t_{HL} \approx 2.2\tau$

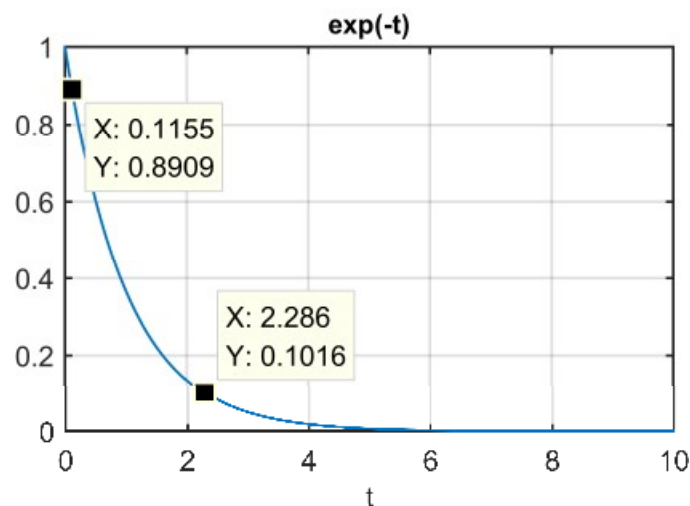

$$t_{HL} = 2.286 - 0.1155 = 2.17$$
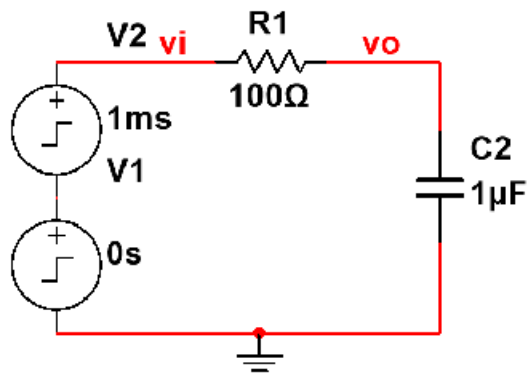
# RC电路充放电仿真

- $\tau = RC = 0.1\text{ms}$ , 仿真时间 $2\text{ms}$  ( $=20 \times \tau$ )



# 信号源设置

STEP\_VOLTAGE

Label Display Value Fault Pins Variant User fields

Initial level: 0 V

Final level: 1 V

Step time: 0 s

Output rise/fall time: 10n s

Replace... OK Cancel Help

STEP\_VOLTAGE

Label Display Value Fault Pins Variant User fields

Initial level: 0 V

Final level: -1 V

Step time: 1m s

Output rise/fall time: 10n s

Replace... OK Cancel Help

# 仿真设置

Transient Analysis

Analysis parameters Output Analysis options Summary

Initial conditions: Determine automatically

Start time (TSTART): 0 s

End time (TSTOP): 0.002 s

☐ Maximum time step (TMAX): Determine automatically s

Setting a small TMAX value will improve accuracy, however the simulation time will increase.

☐ Initial time step (TSTEP): Determine automatically s

Reset to default

Simulate

OK

Cancel

Transient Analysis

Analysis parameters Output Analysis options Summary

Variables in circuit:

All variables

I(C2)  
I(R1)  
I(V1)  
I(V2)  
P(C2)  
P(R1)  
P(V1)  
P(V2)  
V(3)

Filter unselected variables...

Selected variables for analysis:

All variables

V(vi)  
V(vo)

Filter selected variables...

> Add >

< Remove <

Edit expression...

Add expression...

More options

Add device/model parameter...

Delete selected variable

☒ Show all device parameters at end of simulation in the audit trail

Select variables to save

Simulate


OK

Cancel

Help
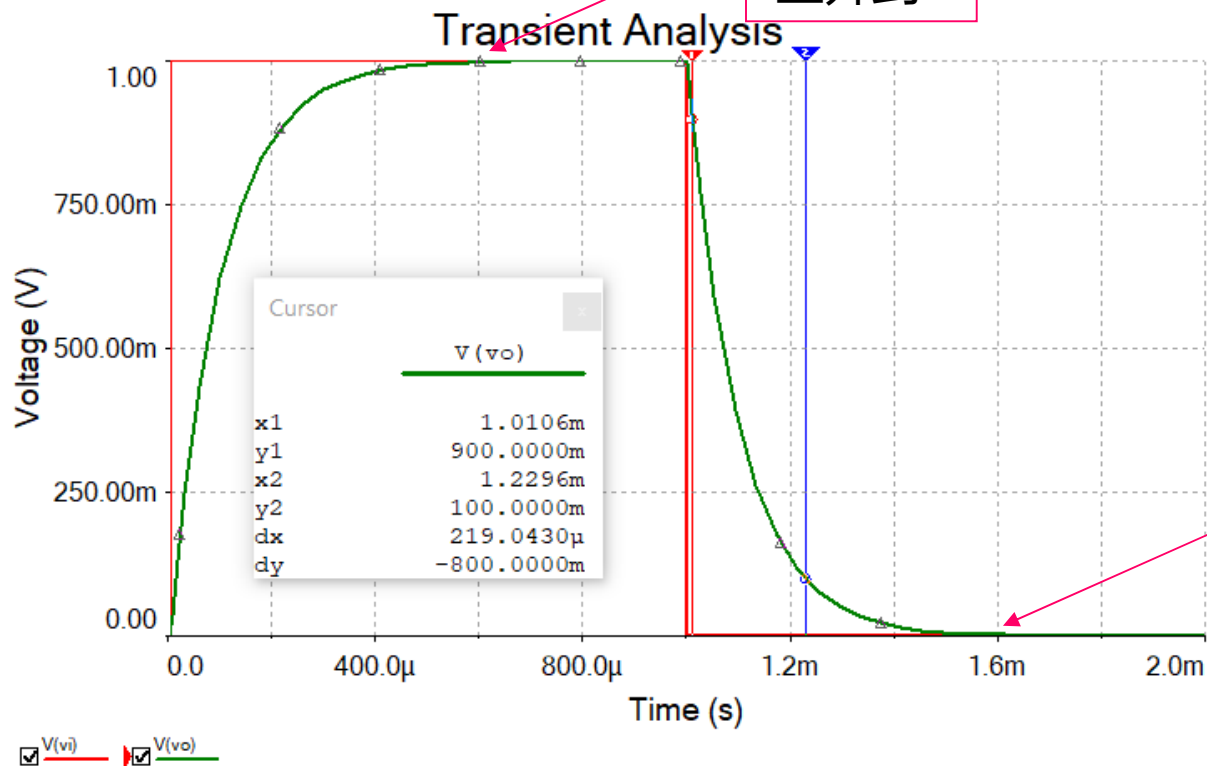
# RC电路充放电仿真

- 0~1ms 充电过程; 1~2ms放电过程
- 放电过程,  $t_{HL}=0.22\text{ms}$  ( $=2.2\tau$ )



0.6ms:  
上升到1

1.6ms:  
下降回0

# 小结

- 电容电压不能突变，RC电路
  - 一方面导致**信号有延迟**，另一方面**波形有失真**
  - 信号延迟的大小与波形失真的程度都与时间常数有关
- 实际电路中寄生电容不可避免
- 对于高速或高频电路，必须通过仿真，确认信号延迟与波形失真是否在可以接受的程度之内