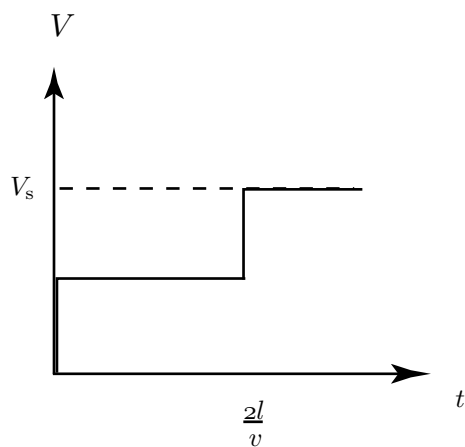



6.630 Solution to Problem Set 5

Solution P5.1

- (a) $t = 2l/v = 4 \text{ ns}$
 (b) The signal quality at the source is poor with two separate transitions to arrive at V_s .



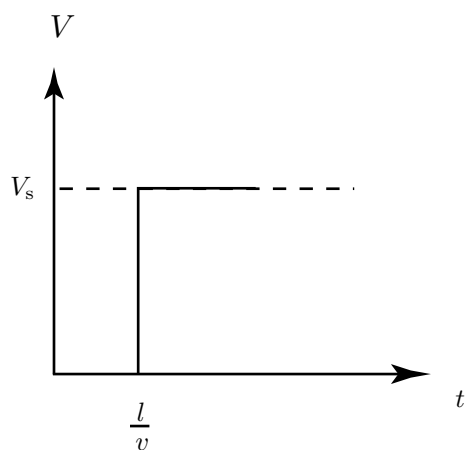- (c) The signal quality at the load is good with a single transition to V_s .




Solution P5.2

- (a) $V_+ = I_o Z_o / 2, V_- = -I_o Z_o / 2$.
 (b) $\Gamma_L = V_- / V_+ = -1$.
 (c) $Z_L = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L} = 0$.

- (d) At $\omega t = \pi/2$, $V(z, t) = \text{Re}\{V(z)e^{j\omega t}\} = I_o Z_o \sin kz$.
 (e) $Z_s = V_s/I_{in} = Z_o$.

Solution P5.3

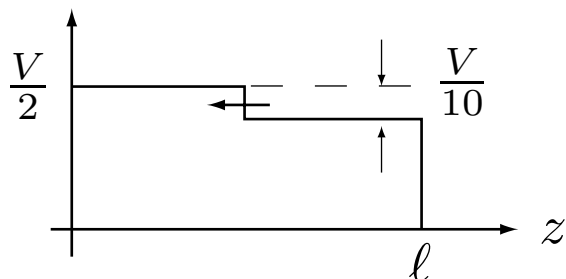- (a) The load of $T1$ is Z_o parallel with $2Z_o$, which is $\frac{2}{3}Z_o$. Therefore the reflection coefficient $\Gamma_L = -\frac{1}{5}$.



- (b) The input impedance of $T3$ is zero since its length is $\lambda/2$ and its load is short. Therefore the input impedance of $T2$ parallel with $T3$ is zero. In other words, the load of $T1$ is short. Therefore Z_{in} for $T1$ is zero.